

214446: DIGITAL LABORATORY

SEIT (2015 Course)

Semester I

Teaching Scheme:-

Practical: 2 Hrs/Week

Theory: 4 Hrs/Week

Examination Scheme:

TW: 25 Marks

Practical: 50 Marks

LABORATORY MANUAL V 7.0

DEPARTMENT OF INFORMATION TECHNOLOGY

2016-2017

Document Control

	Author	Authorizer
Signature		
Name	Mr. D.T.Varpe	
Designation	Asso. Prof.	

INDEX

Sr. No.	Title	Page No.
Group A : Combinational circuit design		
1	Design & implement 4 bit Code Converter.....	21
	a. BCD to Excess-3	
	b. Excess-3 to BCD	
2	Design & implement BCD & Excess 3 Adder using IC 7483.....	
	a. BCD & Excess 3 Adder using IC 7483(4 bit binary adder)	
3	Study of Multiplexer & Decoder IC's.....	
	a. Verification & cascading of IC 74153 and 74138.	
	b. Realization of Boolean Expressions.	
	c. Combinational circuit design (Full adder and Full subtractor).	
Group B : Sequential Logic Design		
4	Design & implement 3 bit Asynchronous & Synchronous counter	
	a. 3 bit up Asynchronouscounter	
	b. 3 bit down Asynchronouscounter	
	c. 3 bit up Synchronouscounter	
	d. 3 bit down Synchronouscounter	
5	Design & implement Modulus- N counter.....	
	a. Using IC 7490 (BCD counter)	
	b. Using IC 74191 (Binary counter)	
6	Design & implement sequence generator using shift register IC 74194	
Group C : VHDL Programming & simulation		
7	Simulation of 4:1 mux	
	a. Using data flow modeling	
	b. Using structural modeling	
8	Simulation of Full Adder.....	
	a. Using behavioral modeling	
	b. Using structural modeling	
9	Simulation of 3 bit controlled up/down Synchronous counter with preset & clear	
	a. Using data flow modeling	
	b. Using behavioral modeling	

SCHEDULE

Sr. No.	Title	No. Of Hrs.	Week
1.	Introduction to digital laboratory & demonstration of digital trainer kit, IC tester	2	1
2.	Design & implement 4 bit Code Converter.	2	2
3	Design & implement BCD & Excess 3 Adder using IC 7483	2	3
4	Study of Multiplexer & Decoder IC's	2	4
5	Design & implement Asynchronous & Synchronous counter	2	5
6	Design & implement Modulus- N counter	2	6
7	Design & implement sequence generator using shift register IC 74194	2	7
	Repeat turn for Assignments 2 to 7	2	8
	Mid-term Mock & Partial Submission	2	9
	Demonstration of VHDL Programming	2	10
8	Simulation of 4:1 multiplexer	2	11
9	Simulation of Full Adder	2	12
10	Simulation of 3 bit counter	2	13
	Final Mock & submission	2	14

1. Code Converter

Title: Code Converter

Aim: Design and implementation of 4-bit Code converters.

- i) BCD to Excess – 3 Code
- ii) Excess-3 to BCD Code

IC's Used:

IC 7404(Hex INV), 7432 (OR-gate), 7408 (AND-gate), 7486 (Ex-or gate)

Theory:

There is a wide variety of binary codes used in digital systems. Some of these codes are binary-coded -decimal (BCD), Excess-3, Gray, octal, hexadecimal, etc. Often it is required to convert from one code to another. For example the input to a digital system may be in natural BCD and output may be 7-segment LEDs. The digital system used may be capable of processing the data in straight binary format. Therefore, the data has to be converted from one type of code to another type for different purpose. The various code converters can be designed using gates.

1. BCD Code:

Binary Coded Decimal (BCD) is used to represent each of decimal digits (0 to 9) with a 4-bit binary code. For example $(23)_{10}$ is represented by 0010 0011 using BCD code rather than $(10111)_2$. This code is also known as 8-4-2-1 code as 8421 indicates the binary weights of four bits (2^3 , 2^2 , 2^1 , 2^0). It is easy to convert between BCD code numbers and the familiar decimal numbers. It is the main advantage of this code. With four bits, sixteen numbers (0000 to 1111) can be represented, but in BCD code only 10 of these are used. The six code combinations (1010 to 1111) are not used and are invalid.

Applications: Some early computers processed BCD numbers. Arithmetic operations can be performed using this code. Input to a digital system may be in natural BCD and output may be 7-segment LEDs.

It is observed that more number of bits are required to code a decimal number using BCD code than using the straight binary code. However in spite of this disadvantage it is very convenient and useful code for input and output operations in digital systems.

 


Fig. 3 BCD Coded Decimal Representation

2. EXCESS-3 Code:

Excess-3, also called XS3, is a non-weighted code used to express decimal numbers. It can be used for the representation of multi-digit decimal numbers as can BCD. The code for each decimal number is obtained by adding decimal 3 and then converting it to a 4-bit binary number. For e.g. decimal 2 is coded as $0010 + 0011 = 0101$ in Excess-3 code.

This is self-complementing code which means 1's complement of the coded number yields 9's complement of the number itself. Self-complementing property of this helps considerably in performing subtraction operation in digital systems, so this code is used for certain arithmetic operations.

BCD To Excess – 3 Code Conversion:

Convert BCD 2 i. e. 0010 to Excess – 3 code

For converting 4 bit BCD code to Excess – 3, add 0011 i. e. decimal 3 to the respective code using rules of binary addition.

$$0010 + 0011 = 0101 - \text{Excess} - 3 \text{ code for BCD } 2$$

Excess – 3 Code To BCD Conversion:

The 4 bit Excess-3 coded digit can be converted into BCD code by subtracting decimal value 3 i.e. 0011 from 4 bit Excess-3 digit.

e.g. Convert 4-bit Excess-3 value 0101 to equivalent BCD code.

$$0101 - 0011 = 0010 - \text{BCD for } 2$$

A. BCD To Excess-3 Code Conversion: Truth Table:

INPUT (BCD CODE)				OUTPUT (EXCESS-3 CODE)			
B ₃	B ₂	B ₁	B ₀	E ₃	E ₂	E ₁	E ₀
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0
1	0	1	0	x	x	x	x
1	0	1	1	x	x	x	x
1	1	0	0	x	x	x	x
1	1	0	1	x	x	x	x
1	1	1	0	x	x	x	x
1	1	1	1	x	x	x	x

2) K-Map For Reduced Boolean Expressions Of Each Output:

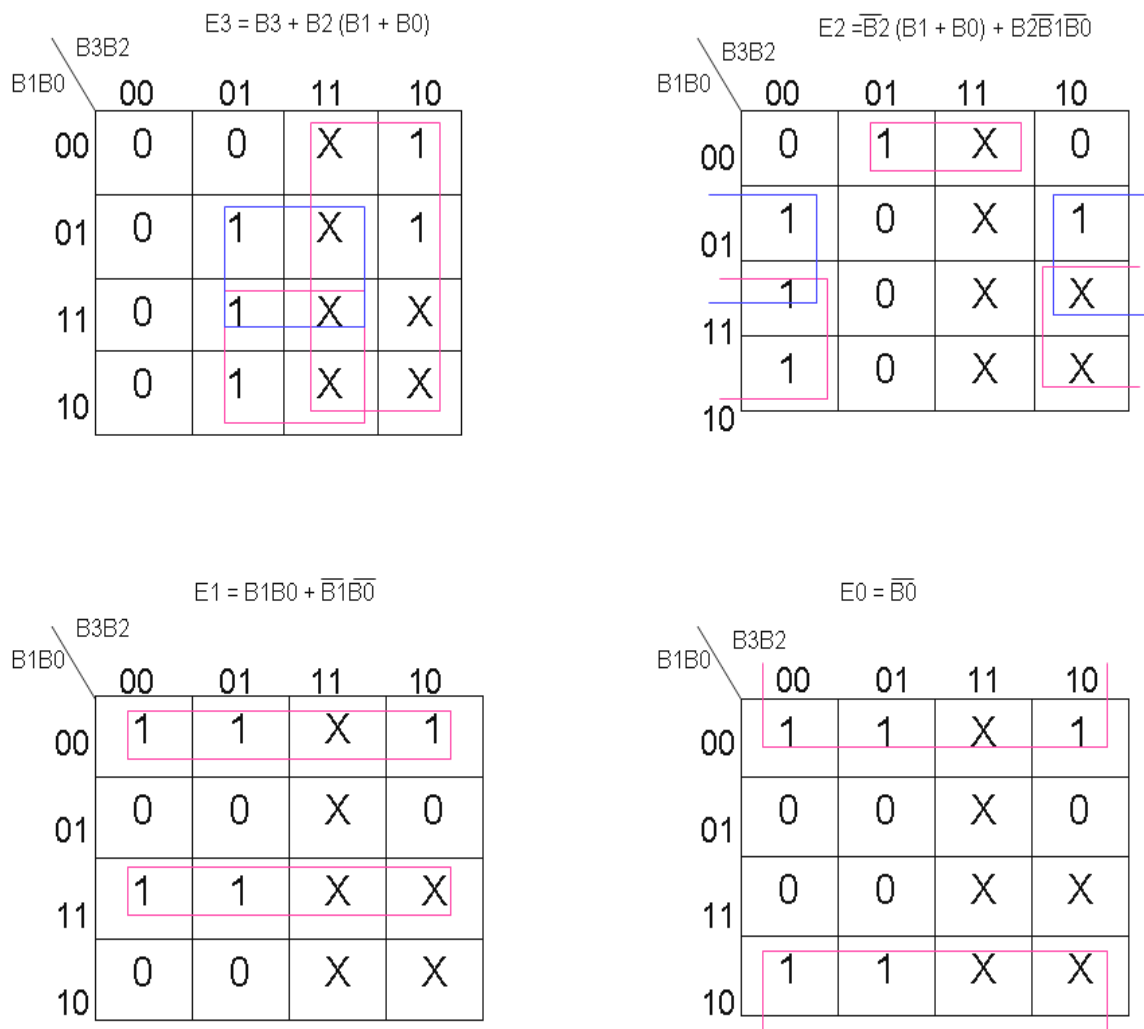


Fig. 8 K-Map For Reduced Boolean Expressions Of Each Output (Excess-3 Code)

3) Circuit Diagram:

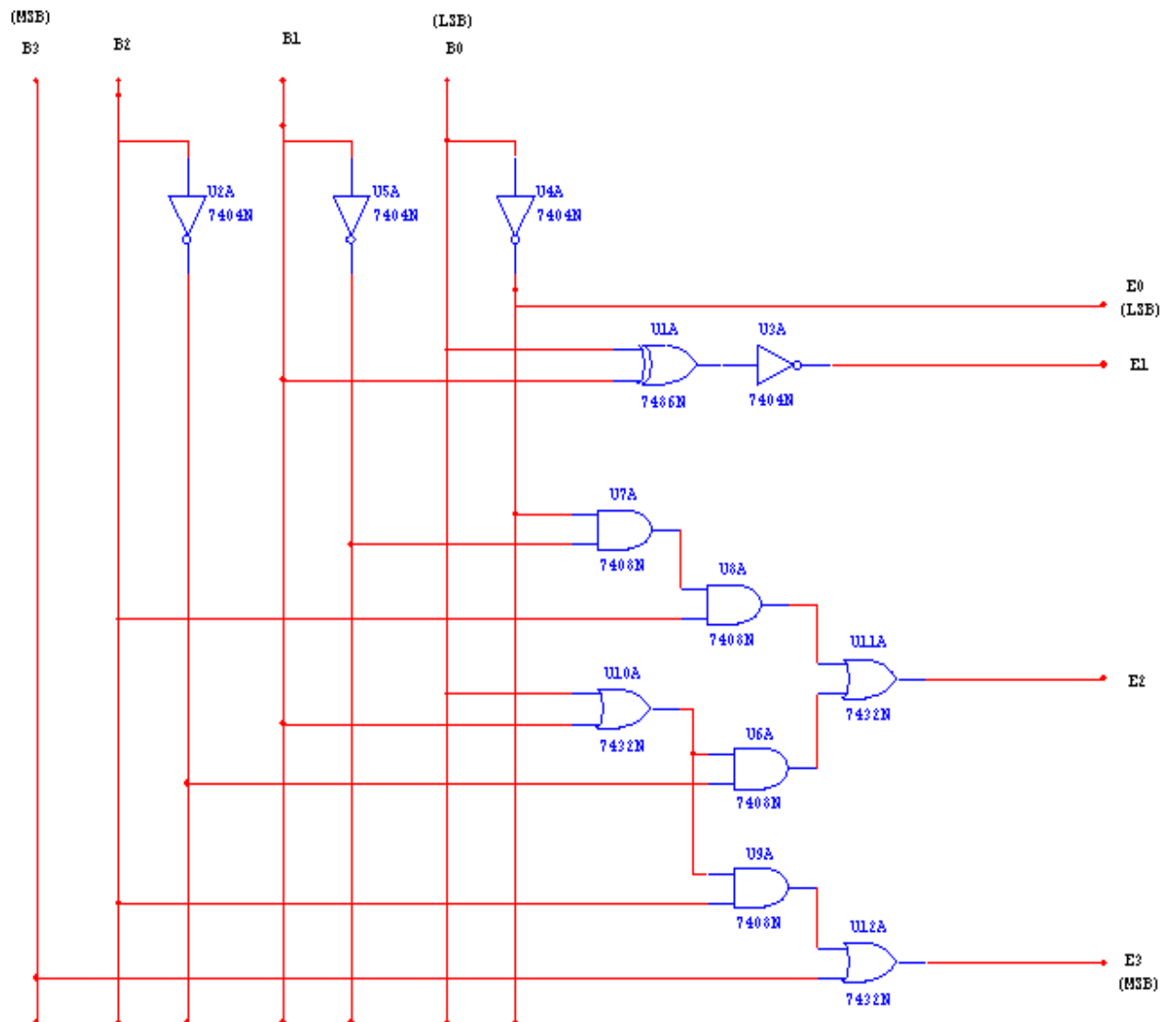
BCD TO EXCESS-3 CONVERTER

Fig.9 Logic Diagram for BCD to Excess-3 Code Conversion

4) Hardware Requirements Table:

GATE	Quantity	IC	Quantity
XOR	1	7486	1
NOT	4	7404	1
AND	4	7408	1
OR	3	7432	1

Table 5 Hardware Requirement Table

B. Excess-3 To BCD Conversion: Truth Table:

INPUT (EXCESS-3 CODE)				OUTPUT (BCD CODE)			
E ₃	E ₂	E ₁	E ₀	B ₃	B ₂	B ₁	B ₀
0	0	0	0	X	X	X	X
0	0	0	1	X	X	X	X
0	0	1	0	X	X	X	X
0	0	1	1	0	0	0	0
0	1	0	0	0	0	0	1
0	1	0	1	0	0	1	0
0	1	1	0	0	0	1	1
0	1	1	1	0	1	0	0
1	0	0	0	0	1	0	1
1	0	0	1	0	1	1	0
1	0	1	0	0	1	1	1
1	0	1	1	1	0	0	0
1	1	0	0	1	0	0	1
1	1	0	1	X	X	X	X
1	1	1	0	X	X	X	X
1	1	1	1	X	X	X	X

2) K-Map For Reduced Boolean Expressions Of Each Output:

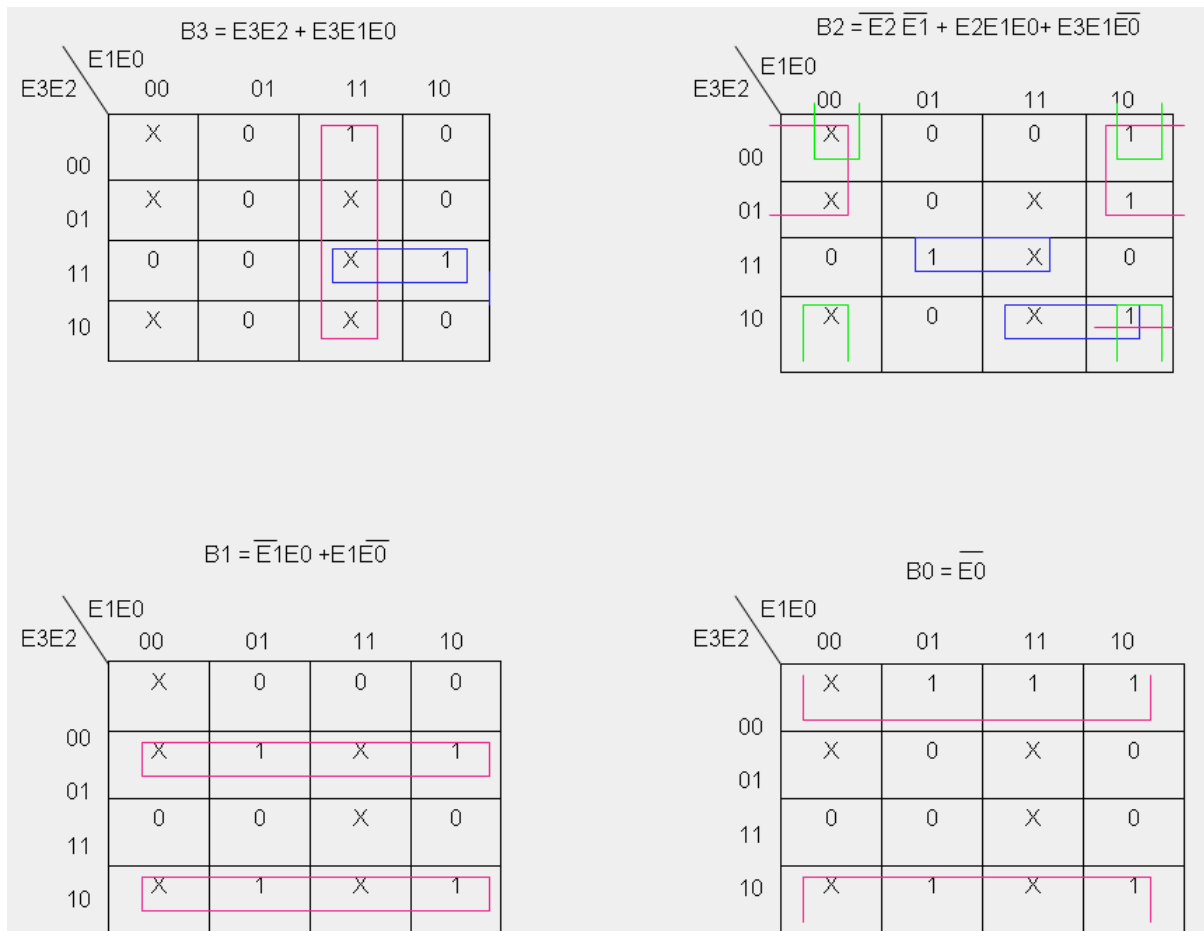


Fig 10 K-Map For Reduced Boolean Expressions Of Each Output (BCD Code)

3) Circuit Diagram:

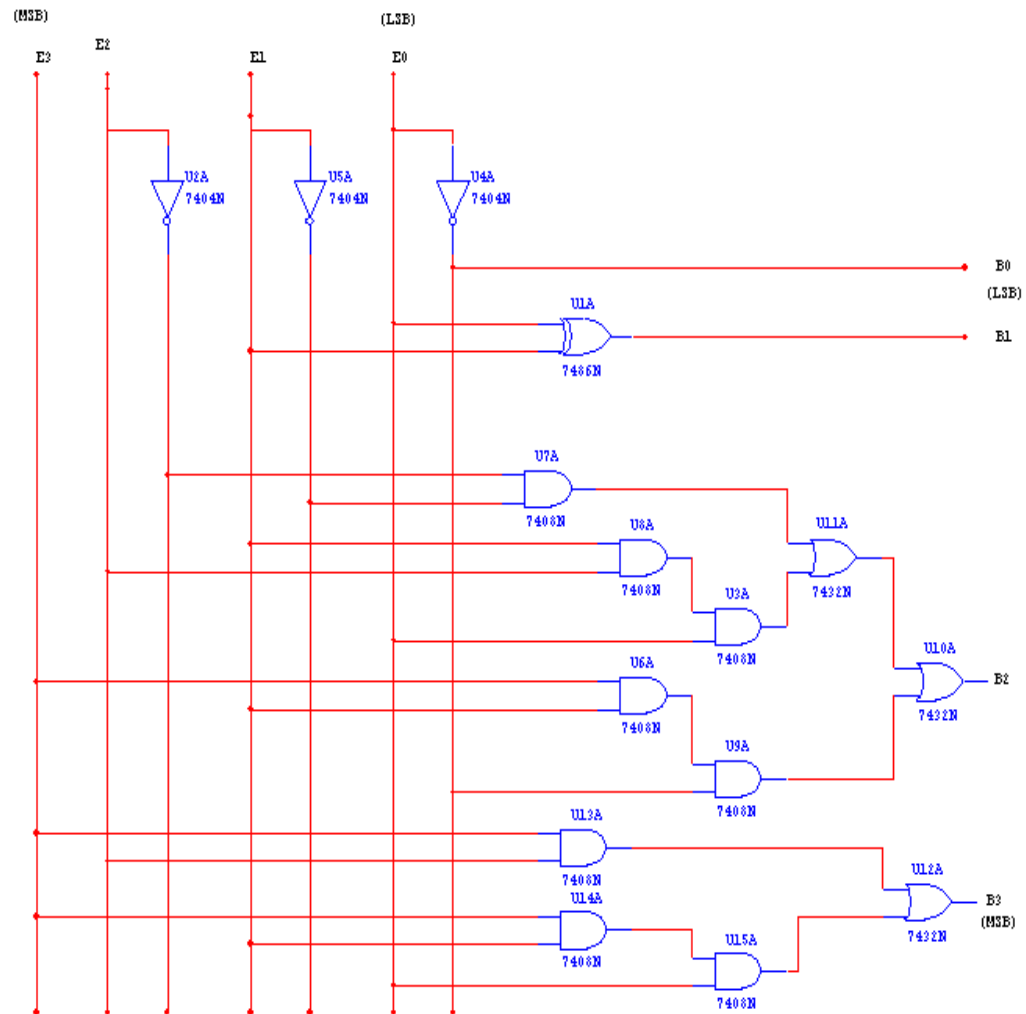
EXCESS-3 TO BCD CONVERTER

Fig.11 Logic Diagram for Excess-3 to BCD Conversion

4) Hardware Requirements Table:

GATE	Quantity	IC	Quantity
XOR	1	7486	1
NOT	3	7404	1
AND	8	7408	2
OR	3	7432	1

Table 5 Hardware Requirement Table

Test the circuit for all possible combinations of input and output codes.

Conclusion:

Thus, we studied different codes and their conversions including applications.

The truth tables have been verified using IC 7486, 7432, 7408, and 7404.

FAQ's with answers:

Q.1) What is the need of code converters?

There is a wide variety of binary codes used in digital systems. Often it is required to convert from one code to another. For example the input to a digital system may be in natural BCD and output may be 7-segment LEDs. The digital system used may be capable of processing the data in straight binary format. Therefore, the data has to be converted from one type of code to another type for different purpose.

Q.2) What is Gray code?

It is a modified binary code in which a decimal number is represented in binary form in such a way that each Gray- Code number differs from the preceding and the succeeding number by a single bit.

(e.g. for decimal number 5 the equivalent Gray code is 0111 and for 6 it is 0101. These two codes differ by only one bit position i. e. third from the left.) It is non weighted code.

Q.3) What is the significance of Gray code?

Important feature of Gray code is it exhibits only a single bit change from one code word to the next in sequence. Whereas by using binary code there is a possibility of change of all bits if we move from one number to other in sequence (e.g. binary code for 7 is 0111 and for 8 it is 1000). Therefore it is more useful to use Gray code in some applications than binary code.

Q.4) What are applications of Gray code?

1. Important feature of Gray code is it exhibits only a single bit change from one code word to the next in sequence. This property is important in many applications such as Shaft encoders where error susceptibility increases with number of bit changes between adjacent numbers in sequence.
2. It is sometimes convenient to use the Gray code to represent the digital data converted from the analog data (Outputs of ADC).
3. Gray codes are used in angle-measuring devices in preference to straight forward binary encoding.
4. Gray codes are widely used in K-map

Q.5) What are weighted codes and non-weighted codes?

In weighted codes each digit position of number represents a specific weight. The codes 8421, 2421, and 5211 are weighted codes. Non weighted codes are not assigned with any

1. Code Converter

weight to each digit position i.e. each digit position within the number is not assigned a fixed value. Gray code, Excess-3 code are non-weighted code.

Q.6) Why is Excess-3 code called as self-complementing code?

Excess-3 code is called self-complementing code because 9's complement of a coded number can be obtained by just complementing each bit.

Q.7) What is invalid BCD?

With four bits, sixteen numbers (0000 to 1111) can be represented, but in BCD code only 10 of these are used as decimal numbers have only 10 digits from 0 to 9. The six code combinations (1010 to 1111) are not used and are invalid.

2. BCD & Excess 3 Adder

AIM : To design & implement of single digit BCD & Excess adder using IC 7483.

OBJECTIVE: 1. To study the BCD arithmetic rules.

2. Comparison between binary and BCD codes.

IC's USED:

IC 7483 (4 bit Binary adder), IC 7404 (Hex INV), 7432 (OR-gate), 7408 (AND-gate), 7486 (EX-OR gate)

THEORY:

BCD Adder:

BCD adder is a circuit that adds two BCD digits & produces a sum of digits also in BCD.

Rules for BCD addition:

1. Add two numbers using rules of Binary addition.
2. If the 4 bit sum is greater than 9 or if carry is generated then the sum is invalid. To correct the sum add 0110 i. e. (6)₁₀ to sum. If carry is generated from this addition add it to next higher order BCD digit.
3. If the 4 bit sum is less than 9 or equal to 9 then sum is in proper form.

CASE I : Sum ≤ 9 & carry = 0.

Add BCD digits 3 & 4

$$\begin{array}{r} 1. \quad 0011 \\ + 0100 \\ \hline \end{array}$$

0111

Answer is valid BCD number = (7)_{BCD} & so 0110 is not added.

CASE II : Sum > 9 & carry = 0.

Add BCD digits 6 & 5

$$\begin{array}{r} 1. \quad 0110 \\ + 0101 \\ \hline \end{array}$$

1011

2. BCD & Excess 3 Adder

Invalid BCD (since sum > 9) so 0110 is to be added

$$\begin{array}{r} 2. \quad 1011 \\ + 0110 \\ \hline 10001 \\ | \quad | \\ \hline \end{array}$$

(1 1)BCD

|

Valid BCD result = (11) BCD

CASE III : Sum <= 9 & carry = 1.

Add BCD digits 9 & 9

$$\begin{array}{r} 1. \quad 1001 \\ + 1001 \\ \hline 10010 \end{array}$$

Invalid BCD (since Carry = 1) so 0110 is to be added

$$\begin{array}{r} 2. \quad 10010 \\ + 0110 \\ \hline 11000 \end{array}$$

(1 8)BCD

Valid BCD result = (18) BCD

Design of BCD adder :

1. To execute first step i. e. binary addition of two 4 bit numbers we will use IC 7483 (with $C_{in} = 0$), which is 4 bit binary adder.
2. We need to design a digital circuit which will sense sum & carry of IC 7483 & if sum exceeds 9 or carry = 1, this digital circuit will produce high output otherwise its output will be zero.

Circuit to check invalid BCD :

First we will design circuit to check sum & then we will logically OR output of this circuit to carry output of IC 7483

For digital circuit which we are going to design we will have 4 inputs (S_3, S_2, S_1, S_0) & only 1 output Y.


a) Y output of this circuit. Will be ORed with carry output of first adder IC 7483.

b) If BCD result is invalid i. e. sum output of first 7483 we have to add $(6)_{10}$ i.e. $(0110)_2$ that means we need one more binary adder IC 7483.

c) If BCD result is valid (i.e. final output of the circuit to check validity is 0) we will make an arrangement that second adder IC 7483 adds $(0)_{10}$ i. e. $(0000)_2$ to the sum of the first adder IC 7483. The output of the combinational circuit is used as final output carry & carry output of second adder IC is ignored.

i) Truth Table for design of combinational circuit for BCD adder to check invalid BCD :

INPUT				OUTPUT
S3	S2	S1	S0	Y
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

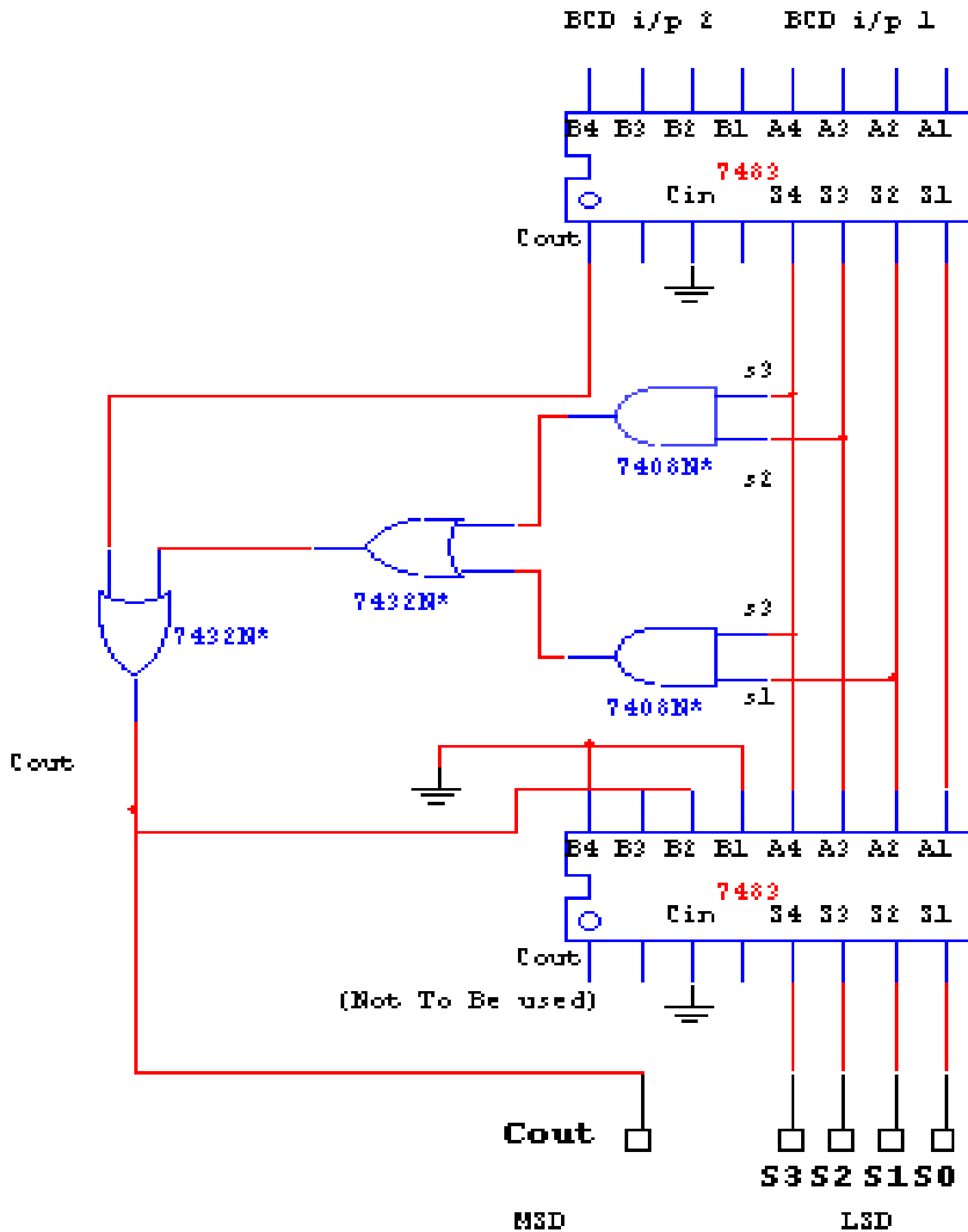iv) Circuit diagram for BCD adder :

v)Hardware Requirements :

GATE	Quantity	IC	Quantity
Binary adder	2	7483	2
AND	2	7408	1
OR	2	7432	1

B) Design and Implement single digit EXCESS-3 adder using IC 7483.

Excess-3 code is a non weighted code. It is a modified form of a BCD code. The Excess-3 code can be derived from the natural BCD code by adding 3 to each coded number. It is also known as Self Complementary code.

Excess-3 code is a self complementary code because 1's complement of Excess-3 number is Excess-3 code for the 9's complement of corresponding number.

Eg: Excess-3 code for $(4)_{10}$ is $(0111)_{XS-3}$. 1's complement of this number is 1000 which is Excess-3 code for $(5)_{10}$ and 5 is 9's complement of $(4)_{10}$.

Rules for Excess-3 addition:

- i. Add two Excess-3 numbers.
- ii. If carry is 1; add 3 to Sum.
- iii. If carry is 0; subtract 3 from sum.

E.g: $(8)_{10} + (6)_{10}$

$(8)_{10} = 1011$ (Excess-3 for 8)

$(6)_{10} = 1001$ (Excess-3 for 6)

```

1 0100
 0011 0011

```

0100 0111 (Excess 3 code for $(14)_{10}$)

(i) Design:

- 1) 4 bit Binary addition of excess 3 codes of two operands can be implemented with IC 7483
- 2) We have to design the circuit which will either add 0011 or subtract 0011 i.e. add 1101 (2's complement of 0011) depending upon carry bit.

Let's compare 0011 and 1101.

B3	B2	B1	B0	
0	0	1	1	----- When carry is 1
1	1	0	1	----- When carry is 0


Here, B0 bit in both situation is High.

Now compare B3, B2 and B1. It is complement of each other.

When carry is 1; Bit B1 =1 B2=B3=0

When carry is 0; Bit B1 =0 B2=B3=1

B1 bit follows the carry and B2 and B3 bit complements the carry.

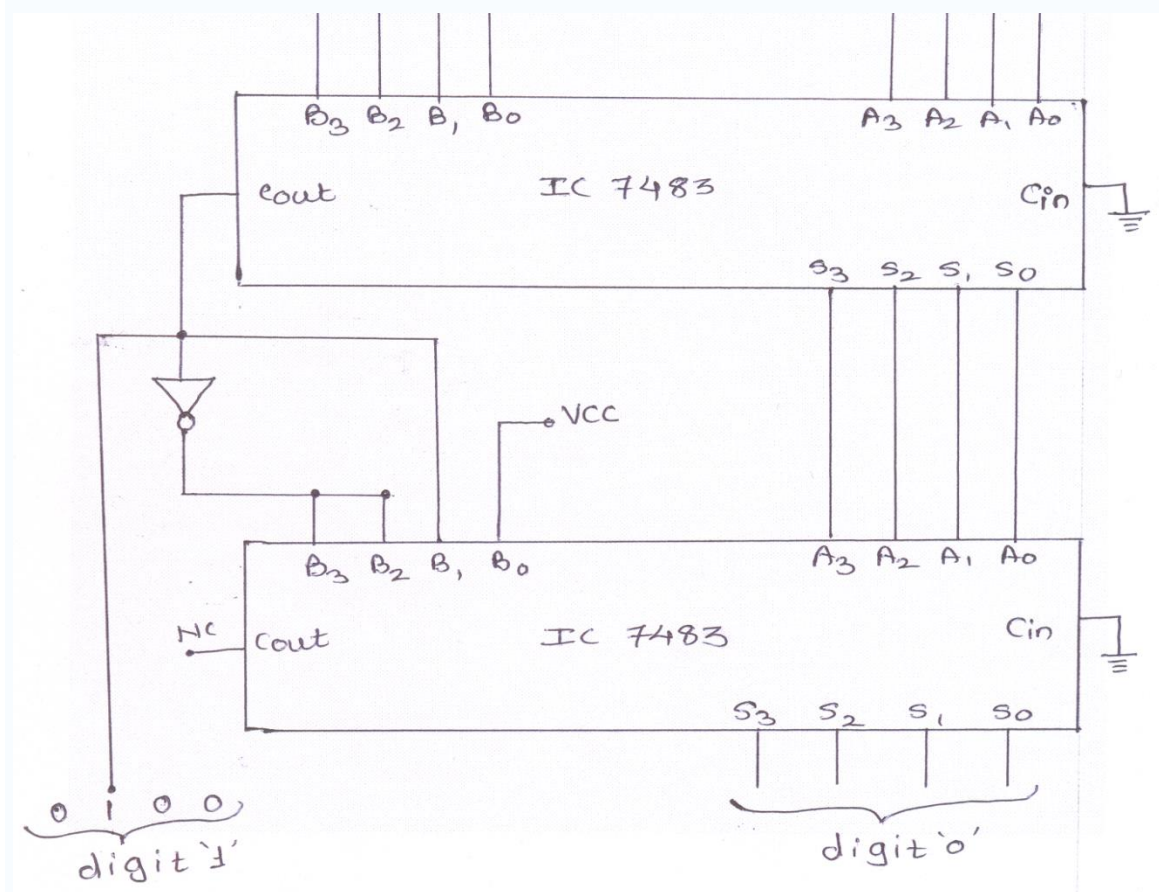(ii) Circuit Diagram:

2. BCD & Excess 3 Adder

(iii) HARDWARE REQUIREMENTS:

Sl No.	IC	Description	Quantity
1	7404	Not Gate	01
2	7483	4 bit Binary Adder	04

OBSERVATION :

BCD adder :

INPUT								OUTPUT				
1 st Operand				2 nd Operand				MSD	LSD			
A3 (MSB)	A2	A1	A0 (LSB)	B3 (MS B)	B2	B1	B0 (LSB)	Cout	S3 (MS B)	S 2	S 1	S0 (LSB)

Excess 3 Adder :

INPUT								OUTPUT							
1 st Operand				2 nd Operand				MSD				LSD			
A3 (MSB)	A2	A1	A0 (LSB)	B3 (MSB)	B2	B1	B0 (LSB)	S7 (MSB)	S6	S5	S4 (LSB)	S3 (MSB)	S2	S1	S0 (LSB)

CONCLUSION :

BCD adder & subtractor is designed & tested for all possible combinations.

FAQ's:

1. Explain and Write the significance of. BCD number system
2. Write the applications of BCD & Excess 3 code.
3. Explain the rules of BCD & Excess 3 arithmetic.
4. What is the difference between BCD and binary codes?
5. What do you mean by unpacked and packed BCD nos.?

PRACTISE ASSIGNMENTS / EXERCISE / MODIFICATIONS:

1. Design & implement two digit BCD adder using IC 7483.
2. Design & implement single digit BCD subtractor using 10's complement method.
3. Design & implement 9's complementer.

3. Study of Multiplexer & Decoder

AIM: Part A – MUX IC 74153

- 1) Verification of IC.
- 2) Implementation of 8:1 Mux by cascading 2, 4:1 mux in IC 74153
- 3) Boolean function implementation
- 4) Full adder implementation using hardware reduction table.

Part B – Decoder IC 74138

- 1) Verification of IC.
- 2) Boolean function implementation.

OBJECTIVE:

1. To study the difference between multiplexer, demultiplexer and decoder.
2. To study the applications of multiplexer.

IC's USED :

IC 74153, 74138, 7404, 7432.

THEORY :

Digital Multiplexer:

Multiplexer are combinational digital circuits equating as controlled switches with several data inputs ($I_0, I_1, I_2 \dots$) & one single data output ("out"). At any time one of the I/p is transmitted to output. According to binary signals applied on control pairs to circuit. Usually the number of data inputs is a power of two.

Multiplexing is the process of transmitting a large no. of information units over a small no. of channel / digital multiplexer is a combinational large circuit which performs the operation of multiplexing. It selects the operation of multiplexing. It selects the operation of binary information from one of the many input lines & transfer to a single o/p line. Multiplexer is called a data selector or multiposition switch because it selects one of the many input. Selection of a particular line is controlled by a set of a selection lines or selects inputs. The number of select lines depends upon no. of input lines.

Generally there is 'n' selects line for 'm' input lines. By applying a particular code on select lines is transmitted on the output lines. Block diagram of

MUX is shown. It contains 2^m input lines 'm' select & one enable input which is used to activate or

3. Study of Multiplexer

dedicate MUX. Depending upon the no. of I/P & O/P lines various types of multiplexers are available. We have 2:1, 4:1, 8:1, 16:1 MUX. Here the first no. indicates the no. of input lines & second no. indicates the no. of output lines.

Demultiplexer :

Demultiplexer is a logic used to perform exactly reverse function performed by multiplexer. It accepts a single input and distributes among several outputs. The selection of a particular output line is controlled by a set of selection line. There are n input lines & 2^m is the number of selection line whose bit combinations determine which output to be selected.

Difference between Multiplexer, Demultiplexer & Decoder

Point	Multiplexer	Demultiplexer	Decoder
Input	Many input lines	Single input line	Many input line also Acts as select line
Output	Single output line	Many output lines	Many output line, Active low output
Select line	$2^m = n$	$n = 2^m$	Enable inputs used

Encoder & Decoder :

1. Encoders are used to encode given digital number into different numbering format .like decimal to BCD Encoder, Octal to Binary.
2. Decoders are used to decode a coded binary word like BCD to seven segment decoder.
3. Thus encoder and decoder are application specific logic develop, we can not use any type of input for any encoder and decoder.
4. Need to select input according to encoder and decoder being selected for a particular application as mention in examples above.

Uses of Mux. :

- 1) Use for Boolean function implementation.

3. Study of Multiplexer

- 2) Construct a common bus system.
- 3) To select between multiple sources & signal destination.
- 4) Inter register transfer.

Advantages :

- 1) Simplification of logic expression not required.
- 2) Logic design is simplified.

Disadvantage :


Only one function can be implemented using one MUX. Hence they can't be used in combinational logic circuit which contains many function.

Part-A (IC 74153)

1. VERIFICATION OF IC 74153 :

IC 74153 is a dual layer 4:1 MUX. It has four input lines for (I_0D - I_3D) for second MUX & active high output. ' Y_a ', ' Y_b ' (1Y or 2Y). It has select lines S_1S_0 common to both MUX. The Enable inputs are active low, E_a & E_b (1G and 2G). The MUX is activated when they are at logic 0.

Pin out of IC 74153:

 

Function table of IC 74153: (X= Don't Care Condition)


			Inputs (I or II)				Output
S_1	S_0	\bar{E} (I or II)	D_0	D_1	D_2	D_3	Y
X	X	1	X	X	X	X	0
0	0	0	0	X	X	X	0
0	0	0	1	X	X	X	1
0	1	0	X	0	X	X	0
0	1	0	X	1	X	X	1
1	0	0	X	X	0	X	0
1	0	0	X	X	1	X	1
1	1	0	X	X	X	0	0
1	1	0	X	X	X	1	1

2.CASCADING OF IC 74153:

Cascading is done to expand two or more MUX IC's to a digital multiplexer with larger no. of inputs i.e. multiplexer stocks or trees is designed. The enable input is used for cascading. In case of IC 74153 we have only two select lines. But for certain application 3 select lines are required then it can be obtained by cascading using enable. Now with 3 select lines we have 8 combinations. Out of this combination the MSB is 0. MSB is 1 for last four combination

so we can use these MSB to select any 1 MUX out of two by connecting it to E pin of first 4:1 MUX .

Logic Diagram

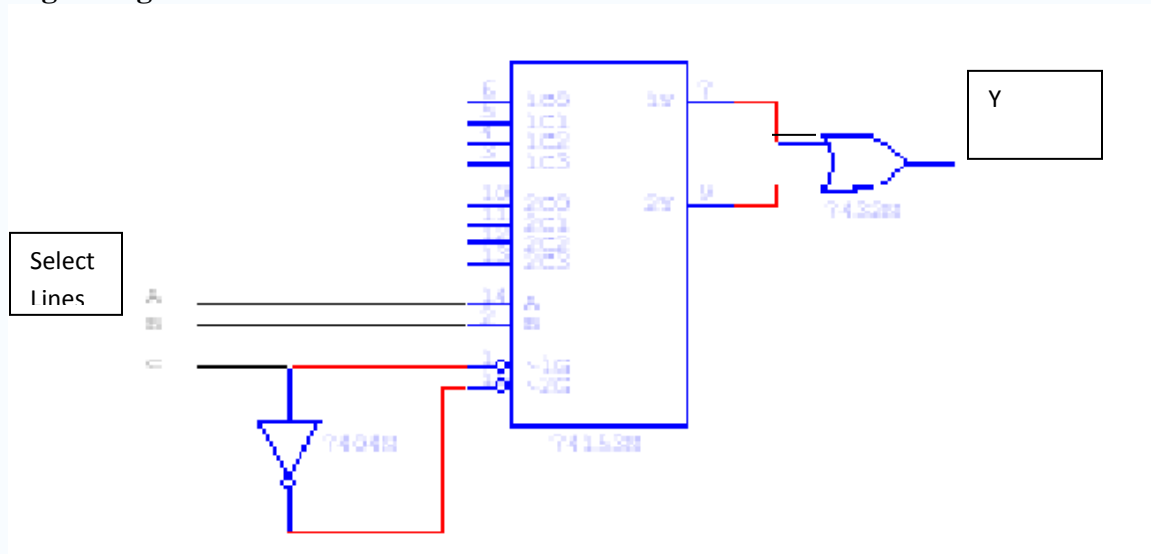

Function table of IC 74153 as 8: 1 Mux by cascading 2 4:1 Mux :

<i>Select Input</i>			<i>Output</i>
<i>C (1G / 2G)</i>	<i>B (S1)</i>	<i>A (S0)</i>	<i>Y</i>
0	0	0	D ₀
0	0	1	D ₁
0	1	0	D ₂
0	1	1	D ₃
1	0	0	D ₄
1	0	1	D ₅
1	1	0	D ₆
1	1	1	D ₇

3.FUNCTION IMPLEMENTATION:


$$Y = \sum m(1, 3, 5, 6)$$

This expression is in Standard SOP form and it is three variable function. So, we need to use mux with three select inputs i.e. 8:1 Mux. Already we have implemented 8:1 Mux using IC 74153. For Boolean function in Standard SOP form we connect data inputs corresponding to the minterms present in the given function to Vcc and remaining data inputs to ground.

Truth table :

<i>Inputs</i>			<i>Output</i>
<i>C</i>	<i>B</i>	<i>A</i>	<i>Y</i>
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

LOGIC DIAGRAM :

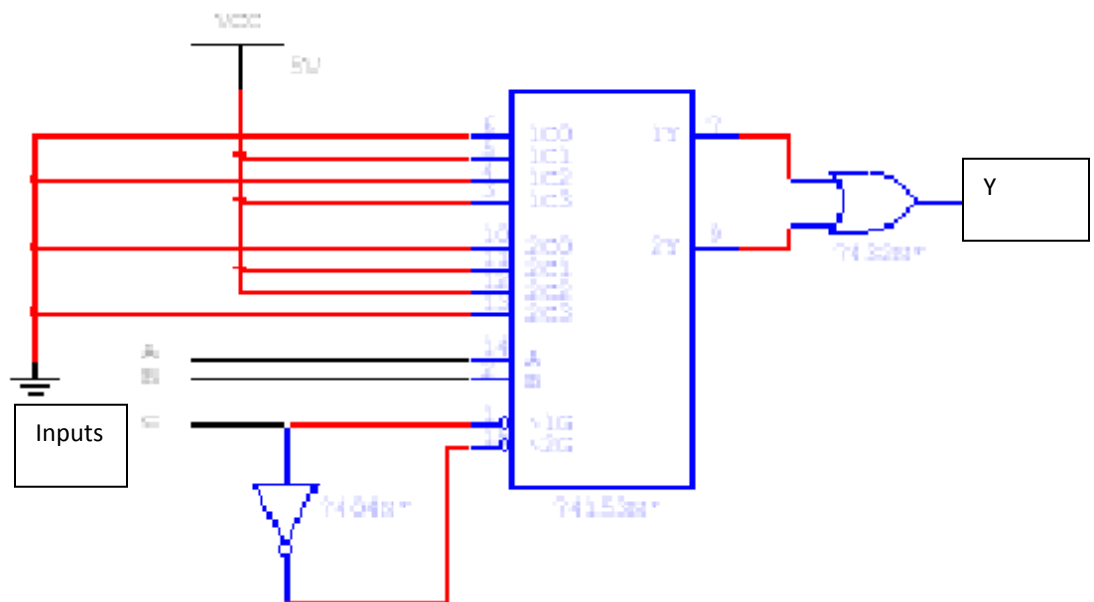

Hardware Requirements :

GATE	Quantity	IC	Quantity
Mux.	1	74153	1
NOT	1	7404	1
OR	1	7432	1

4. IMPLEMENTATION OF FULL ADDER USING IC 74153:

A full adder is a combinational circuit that forms the arithmetic sum of three input bits. It consists of three inputs and two outputs. Two of these variables denoted by A and B represent the two significant bits to be added. The third input represents the carry from previous lower significant position.

Truth Table for Design of full adder:

<i>Input</i>			<i>Output</i>	
A	B	C	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$\text{Sum} = \sum m(1, 2, 4, 7), \text{ Carry} = \sum m(3, 5, 6, 7)$$


Hardware reduction table for Sum:

	D ₀	D ₁	D ₂	D ₃
A	0	1	2	3
A	4	5	6	7
i/p to MUX	A	A	A	A

Hardware reduction table for Carry:

	D ₀	D ₁	D ₂	D ₃
A	0	1	2	3
A	4	5	6	7
i/p to MUX	0	A	A	1

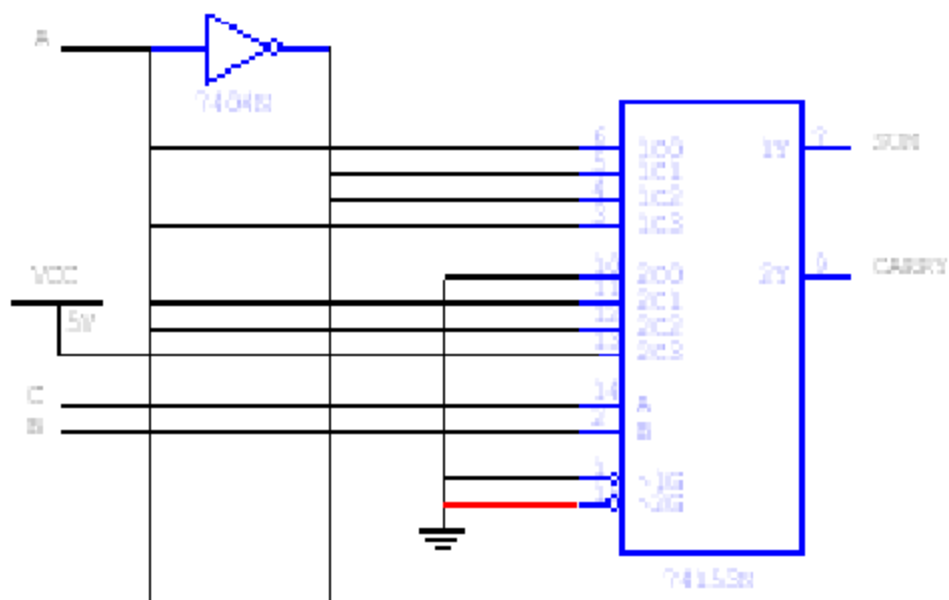Logic Diagram of Full Adder using IC 74153:



Hardware Requirements :

GATE	Quantity	IC	Quantity
Mux.	1	74153	1
NOT	1	7404	1

Part-B Decoder (IC 74138)**THEORY:**

Discrete quantities of information are requested in digital system with binary codes. A binary code of n bits is capable of representing into 2^n distinct elements of the coded information.

Decoder converts coded input to coded outputs accepts one of the code.

There are different types of decoders such as 3:8 decoder, 4:16 line decoders etc. These are in general called as $n:m$ line decoder where $m=2^n$ and n = no. of input lines and m =no. of output lines.

Demux also takes one input data line source and selectively distributes it to one of n output channels. The only difference between demux and decoder is that demux has D_{in} (data i/p) line whereas decoder does not have.

ADVANTAGES:

- 1) The decoder provides best implementation whenever there are many outputs of the combinational circuit and each o/p of the function (or its complement) is required to be expressed with a small no. of minterms.
- 2) The decoder can function as demux. If the Enable i/p line is taken as D_{in} (data i/p) .

DISADVANTAGES:

Since decoder method requires an OR gate for each o/p function, so there is new hardware used. And it is always advisable to use minimum hardware as we come across problems like propagation delay of gates.

APPLICATIONS:

Decoder is worthily used for decoding binary information and memory interfacing. It is used for the implementation of Boolean function.

A) Verification of IC 74138:

We use IC 74138 which accepts 3 binary weighted inputs (A0, A1, A2) and when enabled provides mutually exclusive active low outputs (y0-y7). It features 3 Enable i/ps. Two active low (G2A, G2B) and one active high (G1). Every output will be high unless G2A, G2B are low and G1 is high. It has demultiplexing capability and multiple enable i/ps for easy expansion.

Function Table of 3:8 decoder:

Input						Output							
Enable			Data										
G2A	G2B	G1	A2	A1	A0	Y0	Y1	Y2	Y3	Y4	Y5	Y6	Y7
0	0	0	X	X	X	1	1	1	1	1	1	1	1
0	1	1	X	X	X	1	1	1	1	1	1	1	1
1	0	1	X	X	X	1	1	1	1	1	1	1	1
1	1	1	X	X	X	1	1	1	1	1	1	1	1
0	0	1	0	0	0	0	1	1	1	1	1	1	1
0	0	1	0	0	1	1	0	1	1	1	1	1	1
0	0	1	0	1	0	1	1	0	1	1	1	1	1
0	0	1	0	1	1	1	1	1	0	1	1	1	1
0	0	1	1	0	0	1	1	1	1	0	1	1	1
0	0	1	1	0	1	1	1	1	1	1	0	1	1
0	0	1	1	1	0	1	1	1	1	1	1	0	1
0	0	1	1	1	1	1	1	1	1	1	1	1	0


B) Cascading of IC 74138:

The enable i/p G1 active high of IC 74138 is used for cascading. For cascading 2 IC's, the enable i/p G1 of first IC is connected to G1 enable i/p of second IC through a NOT gate. This enable i/p is used as MSB select i/p line A3. The other three select input lines of both IC's (A0, A1, A2) are also shorted to select input lines of second IC to get single i/p select lines (A0, A1, A2).

The i/p line A3 is used to enable/disable the 2 IC 74138 decoders. When A3=0, first IC is enabled and second is disabled. Thus the first decoder will generate minterms from 0000 to 0111 as o/p and the second decoder will generate nothing. When A3=1, the enable conditions are reversed and thus second decoder IC will generate minterms 1000 to 1111.

Function Table of 4:16 decoder using IC 74138 (3:8 decoder):


Input						Output															
Enable		Data																			
G2A	G2B	A3	A2	A1	A0	Y0	Y1	Y2	Y3	Y4	Y5	Y6	Y7	Y8	Y9	Y10	Y11	Y12	Y13	Y14	Y15
0	1	X	X	X	X	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1
1	0	X	X	X	X	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1
1	1	X	X	X	X	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1
0	0	0	0	0	0	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1
0	0	0	0	0	1	1	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1
0	0	0	0	1	0	1	1	0	1	1	1	1	1	1	1	1	1	1	1	1	1
0	0	0	0	1	1	1	1	1	0	1	1	1	1	1	1	1	1	1	1	1	1
0	0	0	1	0	0	1	1	1	1	0	1	1	1	1	1	1	1	1	1	1	1
0	0	0	1	0	1	1	1	1	1	1	0	1	1	1	1	1	1	1	1	1	1
0	0	0	1	1	0	1	1	1	1	1	1	0	1	1	1	1	1	1	1	1	1
0	0	0	1	1	1	1	1	1	1	1	1	1	0	1	1	1	1	1	1	1	1
0	0	1	0	0	0	1	1	1	1	1	1	1	1	0	1	1	1	1	1	1	1
0	0	1	0	0	1	1	1	1	1	1	1	1	1	1	0	1	1	1	1	1	1
0	0	1	0	1	0	1	1	1	1	1	1	1	1	1	1	0	1	1	1	1	1
0	0	1	0	1	1	1	1	1	1	1	1	1	1	1	1	1	0	1	1	1	1
0	0	1	1	0	0	1	1	1	1	1	1	1	1	1	1	1	1	0	1	1	1
0	0	1	1	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1	0	1	1
0	0	1	1	1	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1	0	1
0	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	0

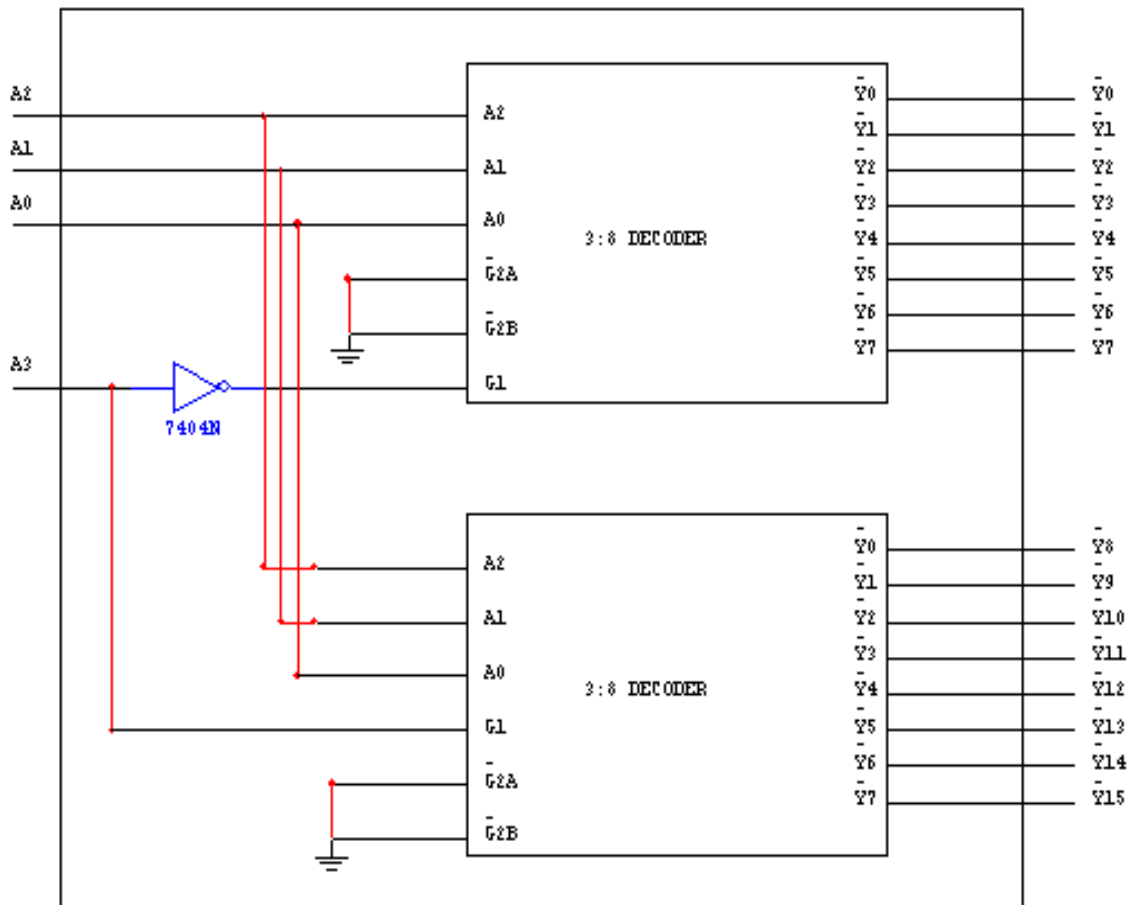

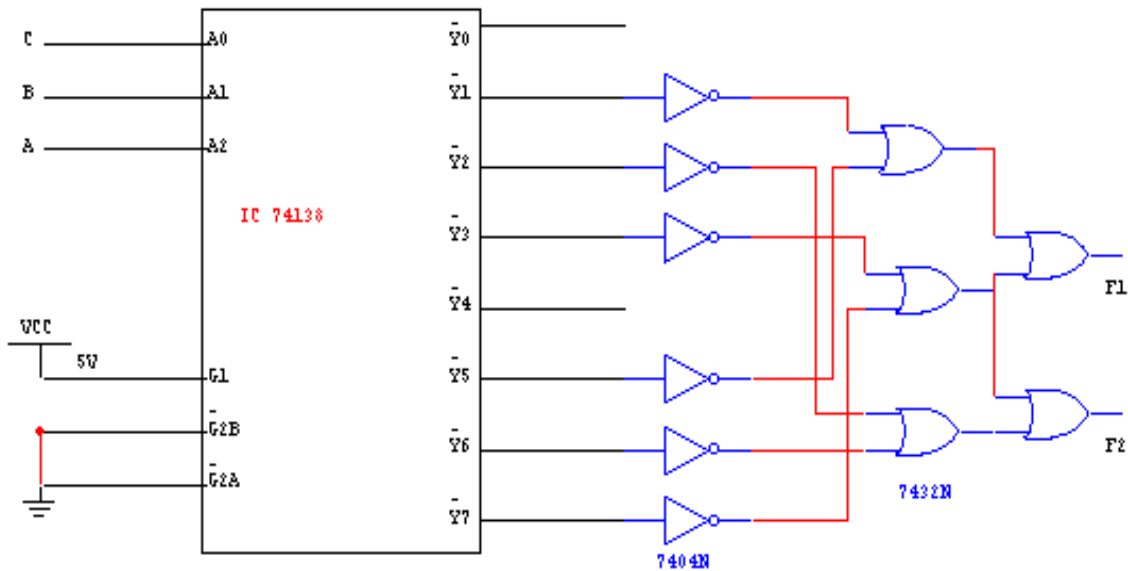C) Implementation of Boolean function:

The procedure for implementation of combinational circuit by means of a decoder and 'OR' gates requires that the Boolean function for the circuit be expressed in Sum of Minterms. These forms can be obtained by expanding the function. A decoder is then chosen which generates all the minterms of n i/p variables. The i/p to each OR gate are selected from the decoder outputs according to the minterms list in each function.

For example, $F1 = \sum m(1, 3, 5, 7)$ and $F2 = \sum m(2, 3, 6, 7)$



D) 1) Implementation of Full Adder:


First of all we need to decide on which type of decoder the above Boolean function can be implemented. The highest minterm is 7 and minimum no. of bits required to represent it in binary form are 3. So we have 3 select lines in 3:8 decoders so we can use IC 74138.

To implement the function we require AND and NAND gate (7408 & 7400). As the o/p of the decoder IC 74138 are active low and we need to get o/p active high at the o/p pin of the function SUM and CARRY when respective minterms are selected.

Truth Table for design of Full Adder:

INPUT			OUTPUT	
A2	A1	A0	SUM	CARRY
A	B	C		
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1
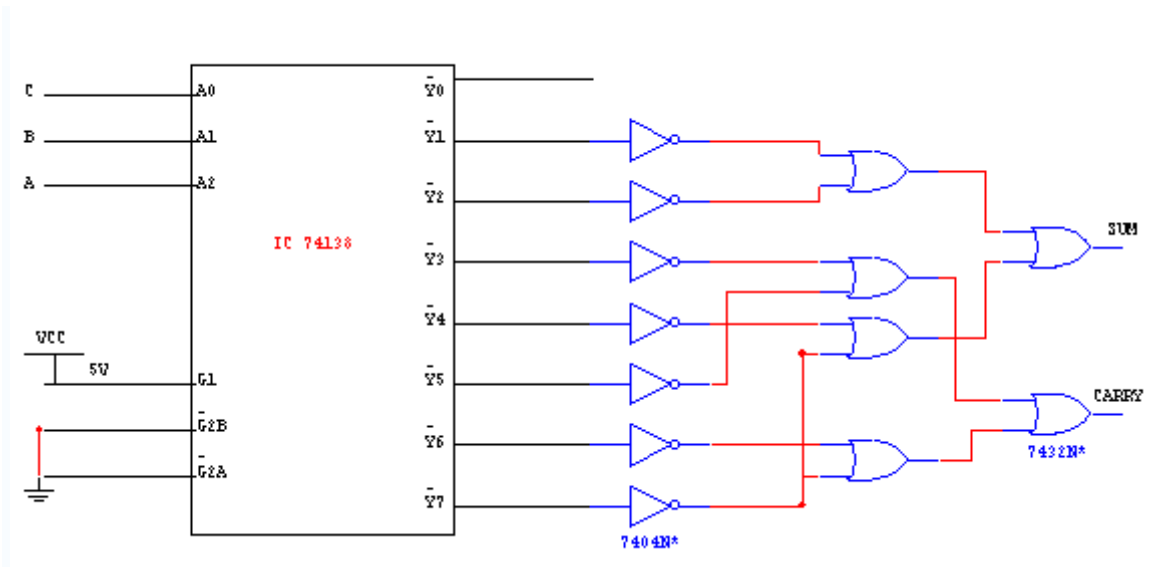
$$\text{SUM} = \sum m(1, 2, 4, 7) \quad \text{CARRY} = \sum m(3, 5, 6, 7)$$



2) Implementation of Full Subtractor:

Same case will happen in this case. Again first of all we need to decide on which type of decoder the above Boolean function can be implemented. The highest minterm is 7 and minimum no. of bits required to represent it in binary form are 3. So we have 3 select lines in 3:8 decoders so we can use IC 74138.


To implement the function we require AND and NAND gate (7408 & 7400). As the o/p of the decoder IC 74138 are active low and we need to get o/p active high at the o/p pin of the function DIFFERENCE and BORROW when respective minterms are selected.

Truth Table for design of Full Subtractor:

INPUT			OUTPUT	
A2	A1	A0	DIFFERENCE	BORROW
A	B	C		
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

$$\text{DIFFERENCE} = \sum m(1, 2, 4, 7)$$

$$\text{BORROW} = \sum m(1, 2, 3, 7)$$

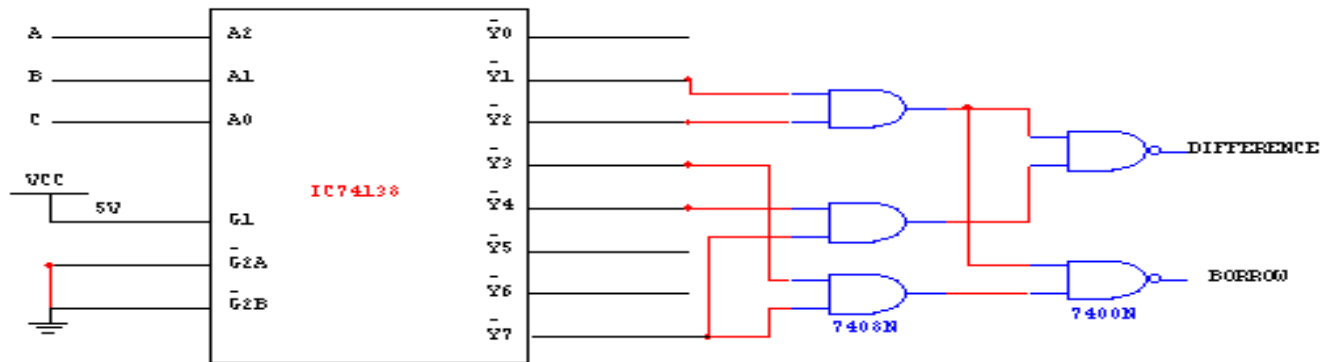

Conclusion : In this way multiplexer, Decoder & its applications are studied, implemented & tested.

FAQ's:

1. What is a multiplexer?
2. What is a Demultiplexer?
3. Enlist applications of multiplexer.
4. Define the terms Encoder and Decoder.
5. What is the difference between multiplexer & demultiplexer?
6. What is the difference between decoder & demultiplexer?

PRACTICE ASSIGNMENTS / EXERCISE / MODIFICATIONS:

1. Implement 16:1 mux by cascading 4, 4:1 mux using IC 74153.
2. Implement full subtractor using hardware reduction table.

4. Counter

AIM:To design and implement 3 bit UP, Down Ripple & Synchronous Counter using MS-JK Flip-flop.

OBJECTIVE:To understand design procedure of asynchronous & Synchronous counter.

ICs USED : IC 7476 (MS-JK Flip-flop), IC 7408(Quad 2 i/p AND Gate),
IC 7432 (Quad 2 i/p OR Gate) and IC 7404 (Hex Inverter).

THEORY:

Counters : counters are logical device or registers capable of counting the no. of states or no. of clock pulses arriving at its clock input where clock is a timing parameter arriving at regular intervals of time, so counters can be also used to measure time & frequencies. They are made up of flip flops. Where the pulse are counted to be made of it goes up step by step & the o/p of counter in the flip flop is decoded to read the count to its starting step after counting n pulse incase of module counters.

Types of Counters:

Counter are of two types:

1) **Asynchronous counter.**

2) **Synchronous counter.**

Asynchronous counter:

A digital counter is a set of flip flop. The flip flop are connected such that their combined state at any time is binary equivalent of total no. of pulses that have occurred up to that time. Thus its name implies a counter is used to count pulse. A counter is used as frequency dividers. To obtain waveform with frequency that is specific fraction of clock frequency.

Counter may be Asynchronous or synchronous. The Asynchronous counter is also called as ripple counter. An Asynchronous counter uses T flip flop to perform a counting function. The actual hardware used is usually J-K flip flop with J & K connected to logic 1. Even D flip flops may be used here.

In asynchronous counter commonly called ripple counter, the first flip-flop is clocked by the external clock pulse & then each successive flip-flop is clocked by the Q or Q' output of the previous flip-flop. Therefore in an asynchronous counter the flip-flop's are not clocked simultaneously. The input of MS-JK is connected to VCC because when both inputs are one output is toggled. As MS-JK is negative edge triggered at each high to low transition the next flip-flop is triggered.

Synchronous Counter :


When counter is clocked such that each flip flop in the counter is triggered at the same time, the counter is called as synchronous counter. The gates propagation delay at reset time will not be present or we may say will not occur.

1) Asynchronous Up Counter:

Fig. 1 shows 3bit Asynchronous Up Counter. Here Flip-flop 2 act as a MSB Flip-flop and Flip-flop 0 act as a LSB Flip-flop. Clock pulse is connected to the Clock of Flip-flop 0. Output of Flip-flop 0(Q₀) is connected to clock of next flip-flop (i.e Flip-flop 1) and so on. As soon as clock pulse changes output is going to change (at the negative edge of clock pulse) as a Up count sequence. For 3 bit Up counter state table is as shown below.

State Table :

Counter States	Count		
	Q ₂	Q ₁	Q ₀
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1
8	0	0	0

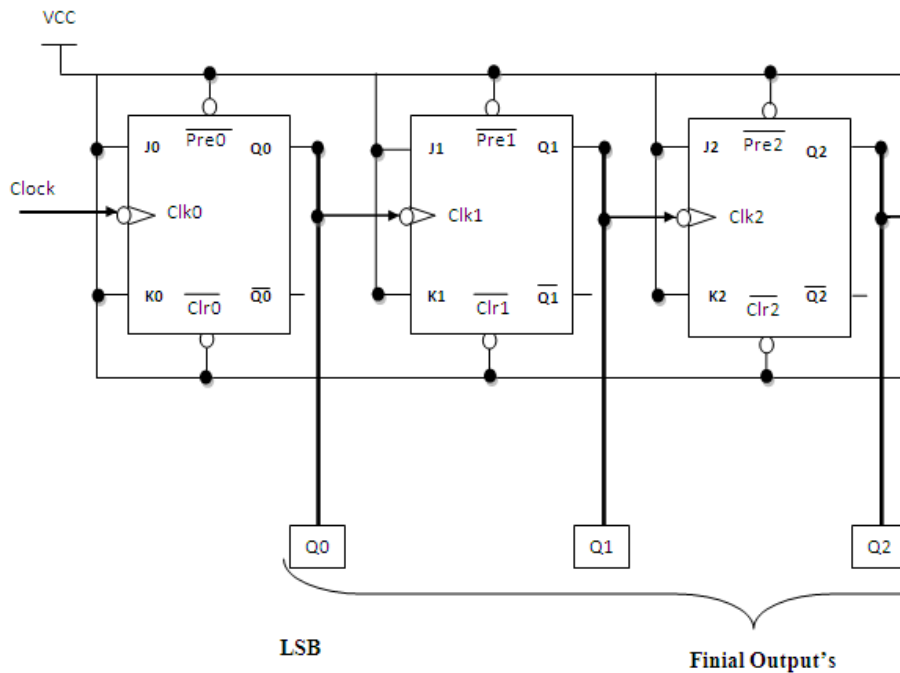Logic diagram :**Fig 1: 3 Bit Asynchronous Up Counter****Hardware requirements :**

Gate / Flip flop	Quantity	IC	Quantity
MS JK	3	7476	2

2) Down Counter:

Fig. 2 shows 2 bit Asynchronous Down Counter. Here Flip-flop 2 act as a MSB Flip-flop and Flip-flop 0 act as a LSB Flip-flop. Clock pulse is connected to the Clock of Flip-flop 0. Output of Flip-flop 0 (Q_0') is connected to clock of next flip-flop (i.e Flip-flop 1) and so on. As soon as clock pulse changes output is going to change (at the negative edge of clock pulse) as a down count sequence. For 3 bit down counter state table is as shown below.

In both the counters Inputs J and K are connected to Vcc, hence J-K Flip flop work in toggle mode. Preset and Clear both are connected to logic 1.

State Table :

Counter States	Count		
	Q ₂	Q ₁	Q ₀
7	1	1	1
6	1	1	0
5	1	0	1
4	1	0	0
3	0	1	1
2	0	1	0
1	0	0	1
0	0	0	0
7	1	1	1

Logic diagram :

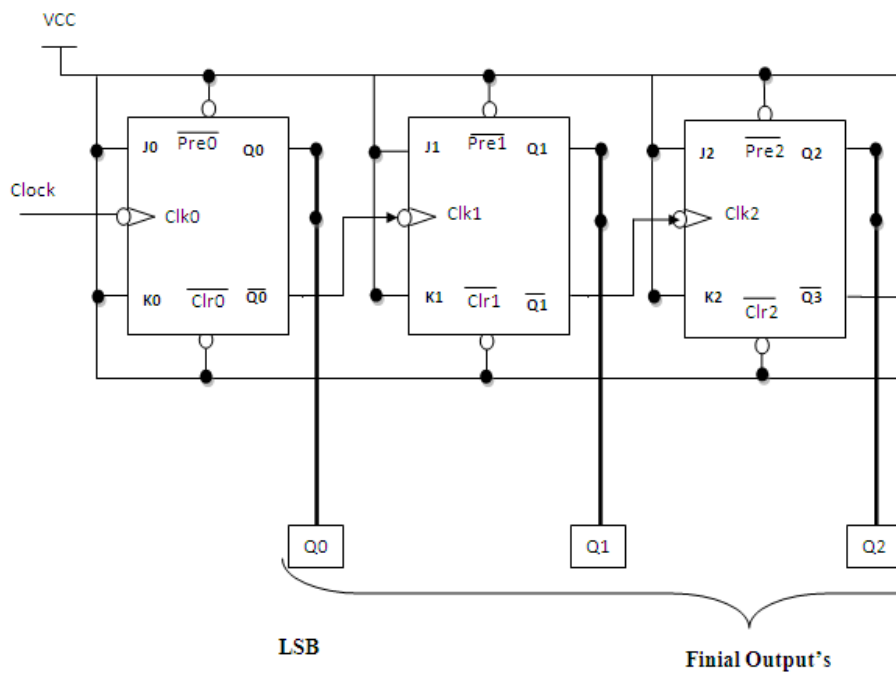


Fig 2: 3 Bit Asynchronous Down Counter

Hardware requirements :

Gate / Flip flop	Quantity	IC	Quantity
MS JK	3	7476	2

Applications :

The asynchronous counters are specially used as the counting devices.

They are also used to count number of pulses applied.

It also works as frequency divider.

It helps in counting the number of product coming out of the machinery where product is coming out at equal interval of time.

Types of synchronous counter:

1) Up counter.

2) Down counter.

1. 3 bit Synchronous up counter:

The up counter counts from 0 to 7 i.e. (000 to 111). For this we are using MS JK flip flop. In IC 74LS76, 2 MS J-K flip flops are present. The clock pulse is given at pin 1 & 6 of the 1st IC & pin 1 of 2nd IC. Next state decoder logic is designed with the help of state table.

State table for synchronous up counter:

Present state			Next state			Flip flop 3		Flip flop 2		flip flop 1	
Q2	Q1	Q0	Q2	Q2	Q0	J2	K2	J1	K1	J0	K0
0	0	0	0	0	1	0	x	0	X	1	x
0	0	1	0	1	0	0	x	1	X	x	1
0	1	0	0	1	1	0	x	x	0	1	x
0	1	1	1	0	0	1	x	x	1	x	1
1	0	0	1	0	1	x	0	0	X	1	X
1	0	1	1	1	0	x	0	1	X	x	1
1	1	0	1	1	1	x	0	x	0	1	X
1	1	1	0	0	0	x	1	x	1	x	1

K-Map :

Q1Q0	00	01	11	10
Q2				
0	0	0	1	0
1	X	X	X	X

$$J_2 = Q_1Q_0$$

Q1Q0	00	01	11	10
Q2				
0	X	X	X	X
1	0	0	1	0

$$K_2 = Q_1Q_0$$

Q1Q0 Q2	00	01	11	10
0	0	1	X	X
1	0	1	X	X

J₁ = Q₀

Q1Q0 Q2	00	01	11	10
0	X	X	1	0
1	X	X	1	0

K₁ = Q₀

Q1Q0 Q2	00	01	11	10
0	1	X	X	1
1	1	X	X	1

J₀ = 1

Q1Q0 Q2	00	01	11	10
0	X	1	1	X
1	X	1	1	X

K₀ = 1

Logic Diagram:

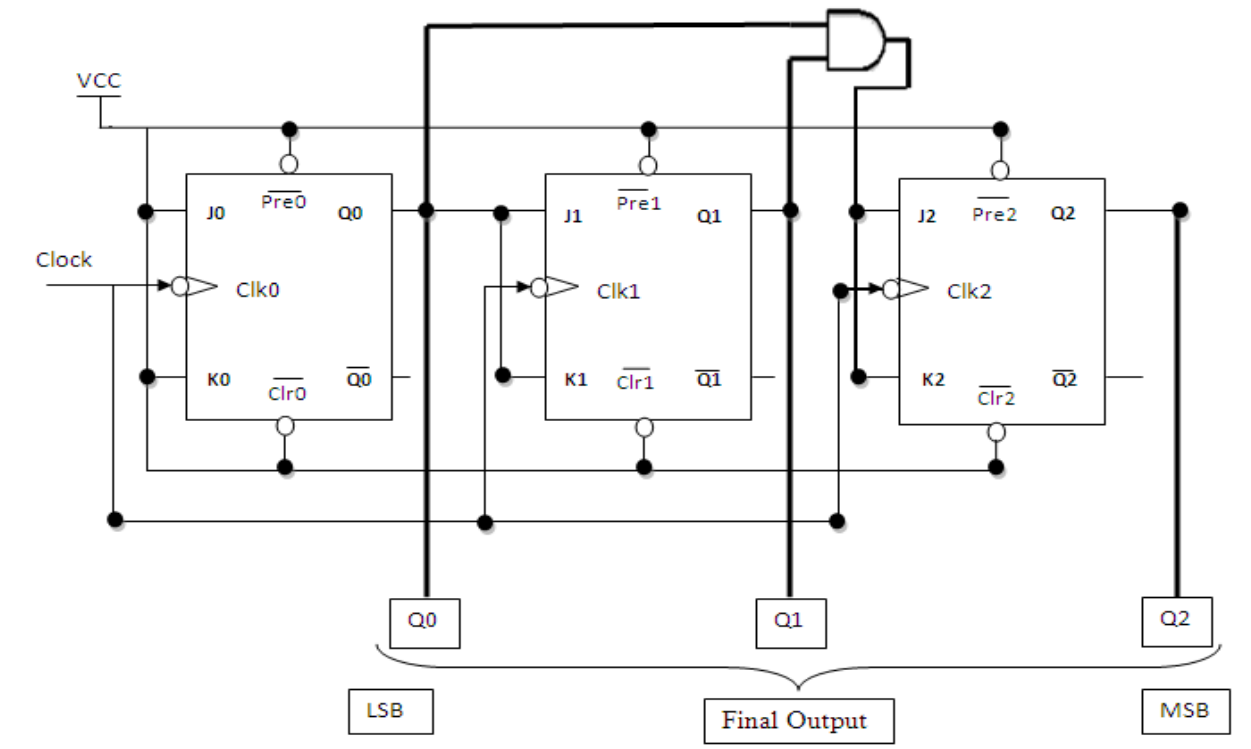


Fig 1: 3 bit Synchronous up counter

2. 3 bit Synchronous down counter:

This is used to count from 7-0 i.e.(111-000).for this also 2 IC's of 74LS76 are required & hence we use 3 MS JK flip flops. Here also clock is given to 1st& 6th pin of 1st IC &1st pin of 2nd IC enabling to apply clock to all flip flop at a time. Next state decoder logic is designed with the help of state table.

State table for synchronous down counter :

Present state			Next state			Flip flop 3		Flip flop 2		Flip flop 1	
Q2	Q1	Q0	Q2	Q1	Q0	J2	K2	J1	K1	J0	K0
1	1	1	1	1	0	X	0	X	0	X	1
1	1	0	1	0	1	X	0	X	1	1	X
1	0	1	1	0	0	X	0	0	X	X	1
1	0	0	0	1	1	X	1	1	X	1	X
0	1	1	0	1	0	0	X	X	0	X	1
0	1	0	0	0	1	0	X	X	1	1	X
0	0	1	0	0	0	0	X	0	X	X	1
0	0	0	1	1	1	1	X	1	X	1	X

K-Map :

Q1Q0	00	01	11	10
Q2				
0	1	0	0	0
1	X	X	X	X

$$J_2 = \underline{Q1Q0}$$

Q1Q0	00	01	11	10
Q2				
0	X	X	X	X
1	1	0	0	0

$$K_2 = \underline{Q1Q0}$$

Q1Q0	00	01	11	10
------	----	----	----	----

Q2				
0	1	0	X	X
1	1	0	X	X

$$J_1 = \underline{Q_0}$$

Q1Q0 \ Q2	00	01	11	10
0	X	X	0	1
1	X	X	0	1

$$K_1 = \underline{Q_0}$$

Q1Q0 \ Q2	00	01	11	10
0	1	X	X	1
1	1	X	X	1

$$J_0 = 1$$

Q1Q0 \ Q2	00	01	11	10
0	X	1	1	X
1	X	1	1	X

$$K_0 = 1$$

Logic Diagram :

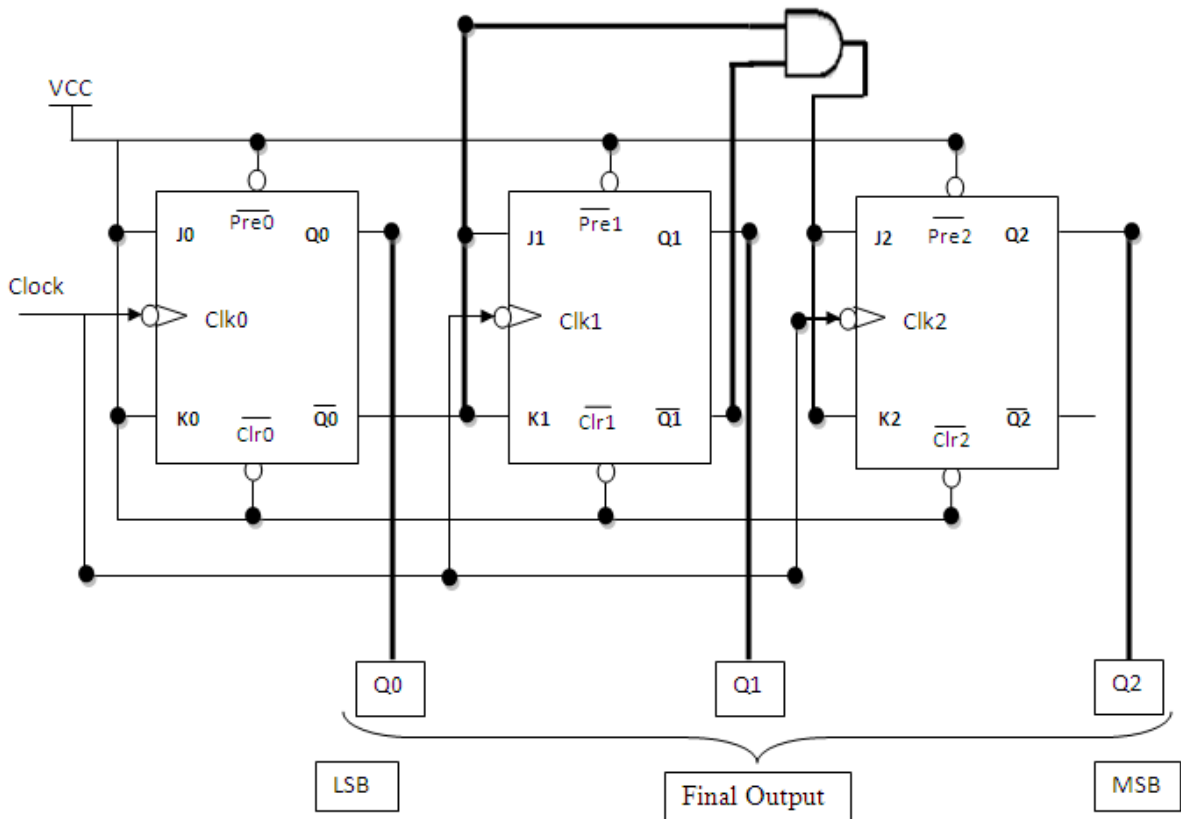


Fig 2: 3 bit Synchronous down counter

Uses:

1. Specially used as the counting devices.
2. Used in frequency divider circuit.
3. Used in digital voltmeter.
4. Used in counter type A to D converter.
5. Used for time measurement..
6. It helps in counting the no of product coming out from machinery where product is coming out at equal interval of time.

Conclusion:

Up and down counters are successfully implemented, the counters are studied & o/p are checked. The state table is verified.

PRACTICE ASSIGNMENTS / EXERCISE / MODIFICATIONS:

1. Design & implement 2 bit controlled synchronous counter.
2. Design& implement 4 bit controlled synchronous counter.
3. Design& implement truncated synchronous up or down counter.

FAQ's with answers:

1. What do you mean by Counter?

A Counter is a register capable of counting the no. of clock pulses arriving at its clock inputs. Count represents the no. of clock pulses arrived. A specified sequence of states appears as the counter output.

2. What are the types of Counters? Explain each.

There are two types of counters as Asynchronous Counter and Synchronous Counter.

Asynchronous Counter: In this counter, the first flip-flop is clocked by the external clock pulse and then each successive flip-flop is clocked by the Q or Q' o/p of the previous flip-flop. Hence in Asynchronous Counter flip-flops are not clocked simultaneously and hence called as Ripple Counter. Synchronous Counter: In this counter, the common clock input is connected to all the flip-flops simultaneously.

3. What do you mean by pre-settable counters?

A counter in which starting state is not zero can be designed by making use of the preset inputs of the flip flops. This is referred to as loading the counter asynchronously. This is referred to as pre-settable counter.

4. What are the applications of synchronous counters?

Digital clock

Frequency divider circuits

Frequency counters

Used in analog to digital converters

5. What are the advantages of synchronous counters over asynchronous counters?

Propagation delay time is reduced.

Can operate at a much higher frequency than the asynchronous counters.

6. Ring counter is an example of synchronous counters or asynchronous counter?

Synchronous counter. Since all the flip flops are clocked simultaneously.

7. Twisted Ring (Johnson's) counter is an example of synchronous counters or asynchronous counter?

Synchronous counter. Since all the flip flops are clocked simultaneously.

8. What is the difference between ring counter and twisted ring counter?

In ring counter pulses to be counted are applied to a counter, it goes from state to state and the output of the flip flops in the counter is decoded to read the count. Here the uncomplimentary output (Q) of last flip flop is fed back as an input to first flip flop. Ring counters are referred as MOD 'N' counters.

But in Twisted ring counter the complimentary output (Q bar) of last flip flop is fed back as an input to first flip flop. Twisted Ring counters are referred as MOD '2N' counters.

9. What are the applications of ring counters?

Ring counter outputs are sequential non-overlapping pulses which are useful for control state counters, Used in stepper motor, this requires pulses to rotate it from one position to the next. Used as divide by 'N' ((MOD 'N') counters.

10. What are the applications of ring counter twisted ring counters?

Used as divide by '2N' ((MOD '2N') counters.

Used for control state counters.

Used for generation of multiphase clock.

11. List the Synchronous Counter ICs.

IC 74160	: Decade Up Counter
IC 74161	: 4 bit binary Up Counter
IC 74162	: Decade Up Counter
IC 74163	: 4 bit binary Up Counter
IC 74168	: Decade Up/Down Counter
IC 74169	: 4 bit Binary Up/Down Counter
IC 74190	: Decade Up/Down Counter
IC 74191	: 4 bit Binary Up/Down Counter
IC 74192	: Decade Up/Down Counter
IC 74193	: 4 bit Binary Up/Down Counter

5. Modulus n Counter

AIM: To design and implement mod - 10, mod - 7, mod - 99 asynchronous BCD counter using IC 7490 and to design and implement up, down, mod - n Binary counter using IC 74191.

OBJECTIVE: To know difference between regular & truncated counter as well as binary & BCD Counter

IC's USED: IC 7490, IC 74191, basic gates.

THEORY: Part A – IC 7490


IC 7490 is a TTL MSI (medium scale integration) decade counter. It contains 4 master slave flip flops internally connected to provide MOD-2 i.e. divide by 2 and MOD-5 i.e. divide by 5 counters. MOD-2 and Mod-5 counters can be used independently or in cascading.

It is a 4-bit ripple type decade counter. The device consists of 4-master slave flip flops internally connected to provide a divide by two and divide by 5 sections. Each section has a separate clock i/p to initiate state changes of the counter on the high to low clock transition.


Since the o/p from the divide by 2 section is not internally connected to the succeeding stages. The device may be operated in various counting modes. In a BCD counter the CP_1 input must be externally connected to Q_A o/p. The CP_0 i/p receives the incoming count producing a BCD count sequence. It is also provided with additional gating to provide a divide by 2 counter and binary counter for which the count cycle length is divide by 5. The device may be operated in various counting modes.

There are 2 reset inputs $R_0(1)$ and $R_0(2)$ both of which need to be connected to the 'logic 1' for clearing all flip flops. Two set inputs $R_g(1)$ and $R_g(2)$ when connected to logic 1 are used for setting counter to 1001 (BCD 9).

Pin out of IC 7490:

 

Basic internal Structure of IC 7490:

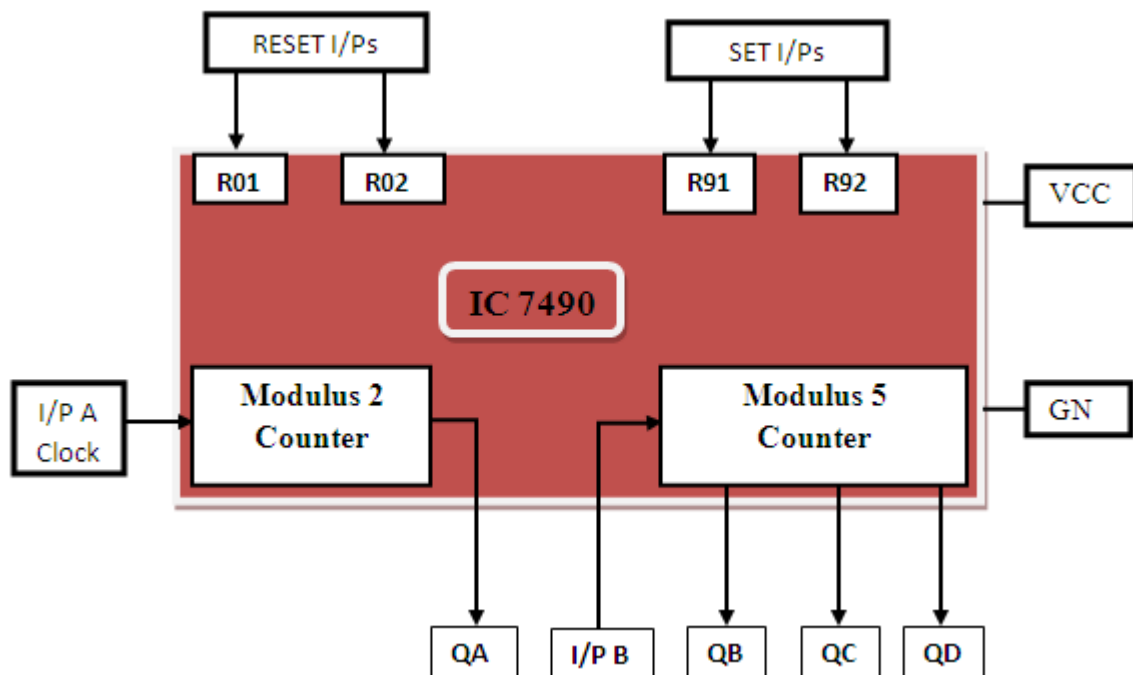

Function Table of MOD-2 counter:

Input A clock	Output	Count
↓	0	0
↓	1	1


Function Table of MOD-5 counter:

InputB clock	Output			Count
	QD	QC	QB	
↓	0	0	0	0
↓	0	0	1	1
↓	0	1	0	2
↓	0	1	1	3
↓	1	0	0	4

Design of MOD-10 counter using IC 7490:

The QA o/p the first flip flop is connected to the input B which is clock i/p of internal MOD-5 ripple counter. Due to cascading of Mod-2 and Mod-5 counters, the overall configuration the decade counters count from 0000 to 1001. After 1001 mod-5 resets to 0000 and next count after 1001 is 0000.


When QA o/p is connected to B i/p, we have the Mod-2 counter followed by Mod-5 counter. The count sequence obtained is shown in the table. It may be noted that QA changes from 0 to 1 the state of Mod-5 counter doesn't change, whereas when QA changes from 1 to 0 the Mod-5 counter goes to the next state.

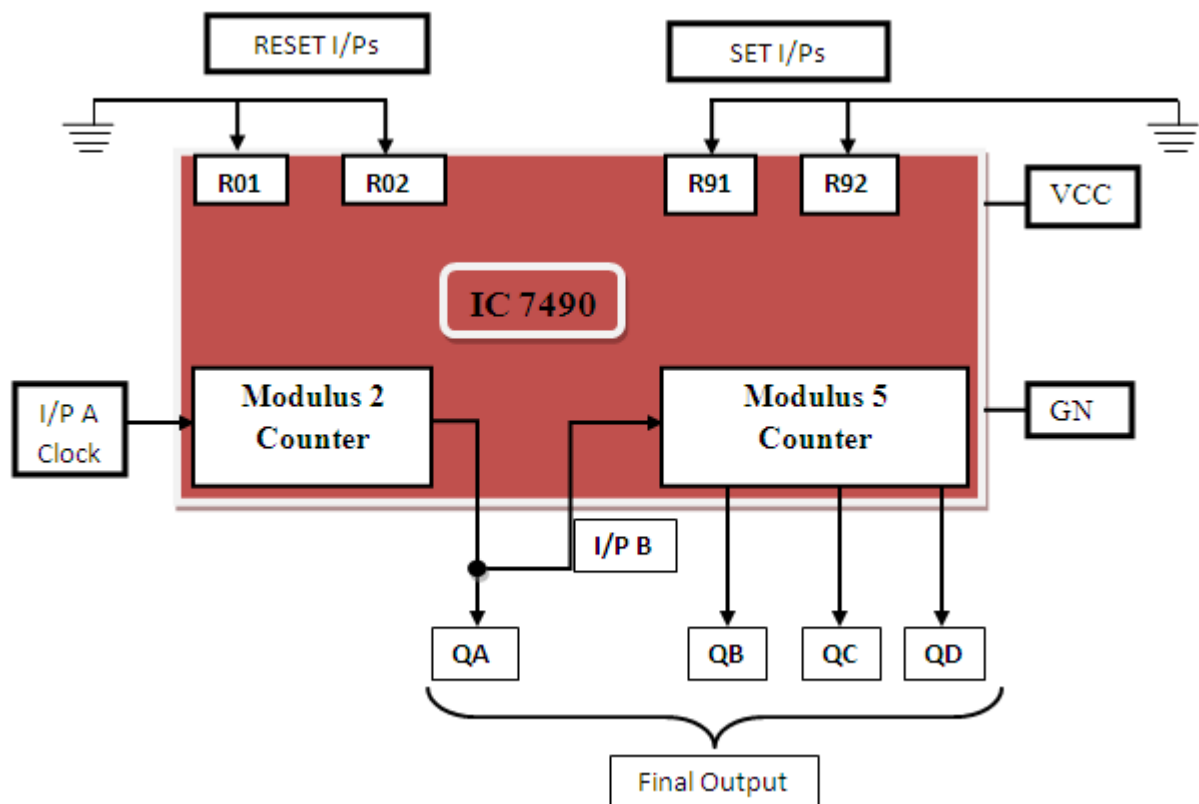Logic Diagram MOD-10 counter using IC 7490:

5. Modulus n Counter

Function table:

I/p clock	Output				Count
	QD	QC	QB	QA	
↓	0	0	0	0	0
↓	0	0	0	1	1
↓	0	0	1	0	2
↓	0	0	1	1	3
↓	0	1	0	0	4
↓	0	1	0	1	5
↓	0	1	1	0	6
↓	0	1	1	1	7
↓	1	0	0	0	8
↓	1	0	0	1	9

 Timing diagram of mod10:**Design of Mod-7 Counter using IC 7490:**


Mod-7 counter counts through seven states from 0 to 6 counters and it should reset as soon as the count becomes 7. The o/p of reset logic should be 1 corresponding to invalid states. The reset logic o/p should be applied to pin 2 and 3.

Truth Table of Reset Logic:

QD	QC	QB	QA	Y
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0

0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1

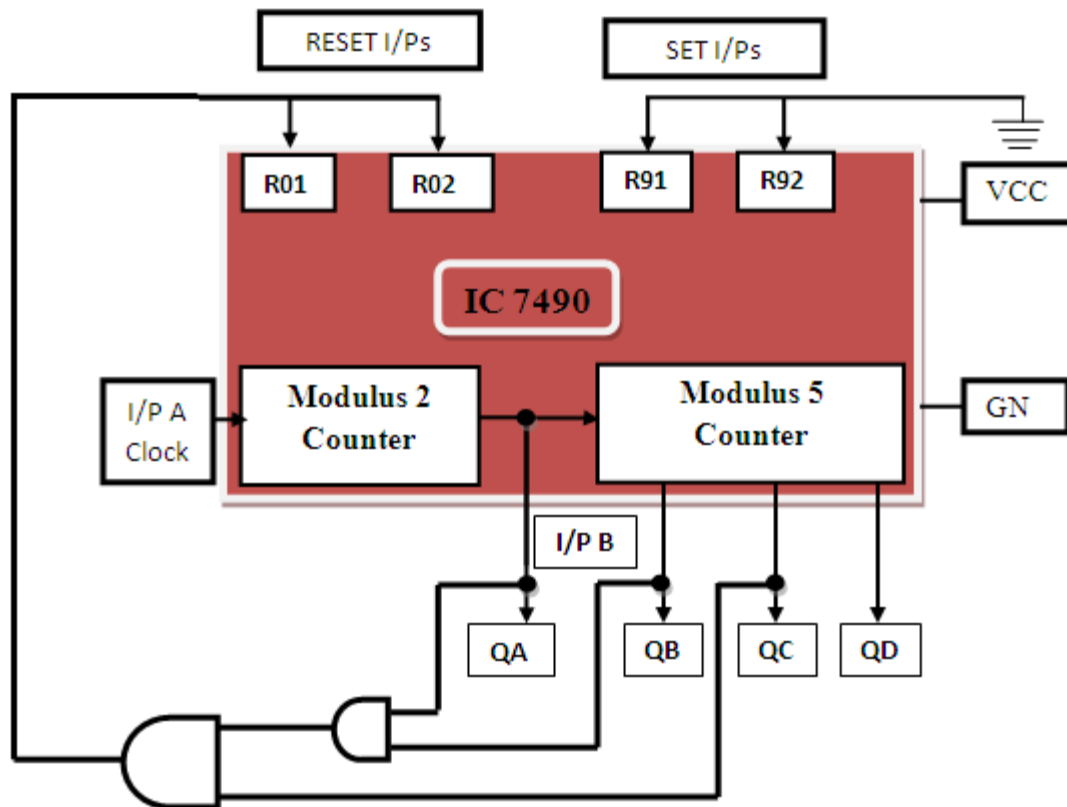Logic Diagram Mod 7 Counter using IC 7490:



5. Modulus n Counter


Function table:

I/p clock	Output				Count
	QD	QC	QB	QA	
↓	0	0	0	0	0

↓	0	0	0	1	1
↓	0	0	1	0	2
↓	0	0	1	1	3
↓	0	1	0	0	4
↓	0	1	0	1	5
↓	0	1	1	0	6


5. Modulus n Counter

Timing diagram of mod7:

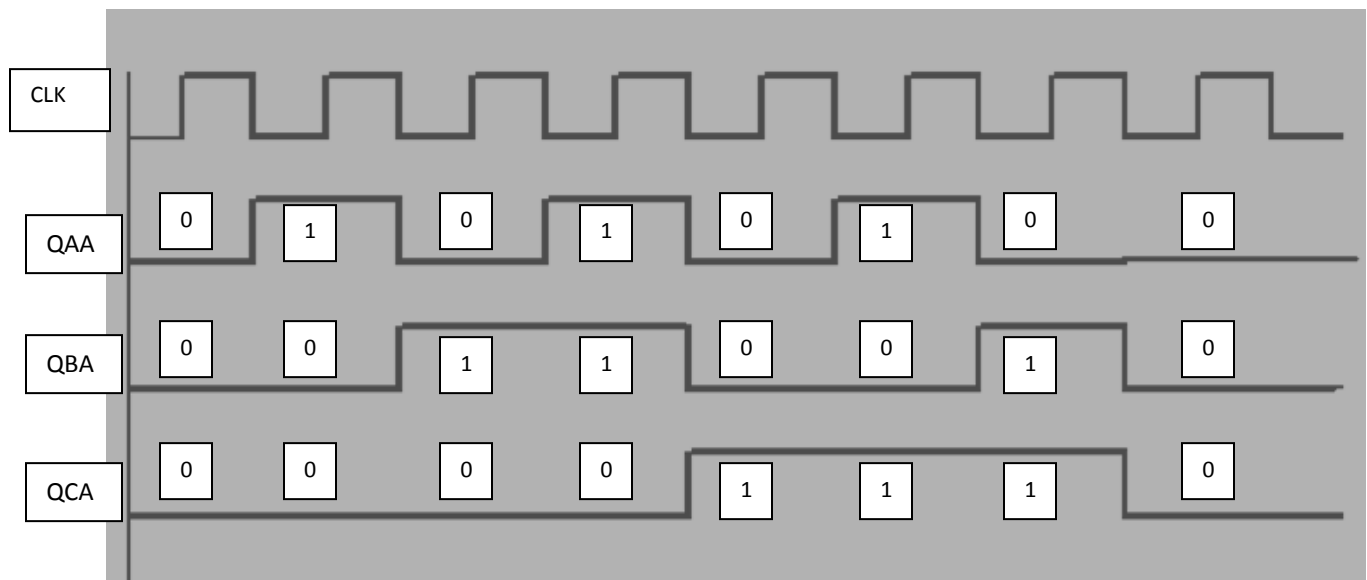

Design of Mod-99 using IC 7490:

For Mod-99 two IC 7490's will be required. Hence to implement a divide by 99 counter we have to use two decade counter IC's. A divide by 99 counter counts 99 states from 0 to 98 and the counter should reset as soon as the count becomes 99. So in order to reset the counter of 99 connect the Q o/p which are equal to 1 in the count of 99 to an 'And' gate & then connect and o/p to the reset i/p of both IC's.

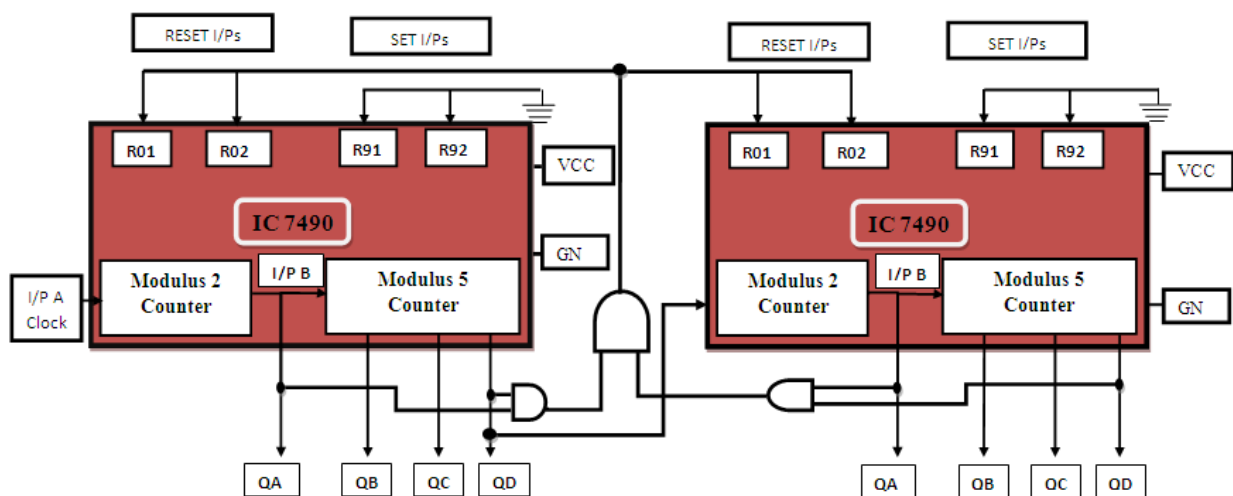

5. Modulus n Counter

B) IC 74191 – Theory

IC74191 is 4-bit binary synchronous, reversible, up down counter. It contains 4 master slave flip flops with internal gating and steering logic to provide asynchronous reset and synchronous count up/down operations, its asynchronous parallel capability permits the counter to be preset to any desire number D0 to D3 are the parallel data inputs. Information present on the parallel data inputs D0 to D3 is loaded into the counter and appears on the output when the load PL input is low. This operation overrides the counting function. Counting is inhibited by the high level on the enable G input, when G input is low internal state changes are initiated synchronously by the low to high transitions of the clock inputs the up/down input signal determines the direction of input.

Function Table :

Operating mode	Inputs					Outputs
	<u>PL</u>	<u>U/D</u>	<u>G</u>	CLK	Dn	
Parallel load	L	X	X	X	L	L
	L	X	X	X	H	H
Count up	H	L	0	↑	X	Count up
Count down	H	H	0	↑	X	Count down
Hold(No change)	H	X	H	X	X	No change

5. Modulus n Counter

Pin details –

D0 to D3 input lines, PL parallel load

G is Enable input – enabling the counting.

Q0 to Q3 output lines.


Down/up determines the direction of counting.

Clk clock input for counter.

Terminal Count : Max(1111) min(0000). For these states signal goes high for 1 clock pulse.

Ripple clock: Clock input for next higher state.

Pin Diagram :

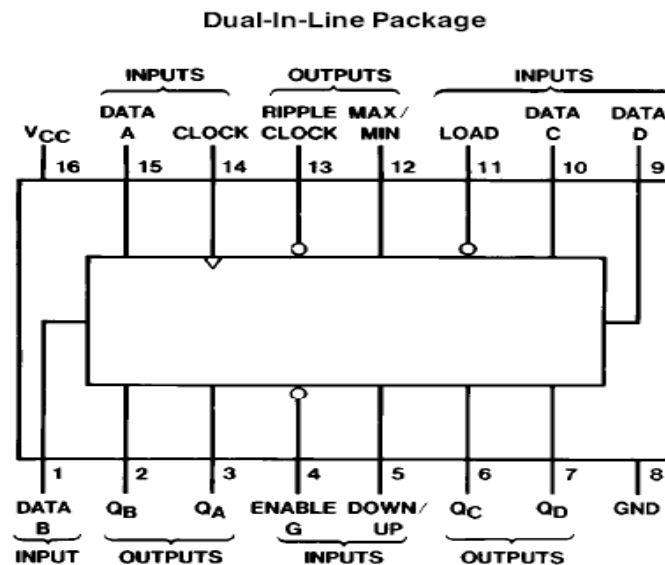


5. Modulus n Counter

Up counter- Truth Table

Clk Pulses	QA	QB	QC	QD
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	1	1	1	1
8	1	0	0	0
9	1	0	0	1
10	1	0	1	0
11	1	0	1	1
12	1	1	0	0
13	1	1	0	1
14	1	1	1	0
15	1	1	1	1

5. Modulus n Counter

Logic Diagram

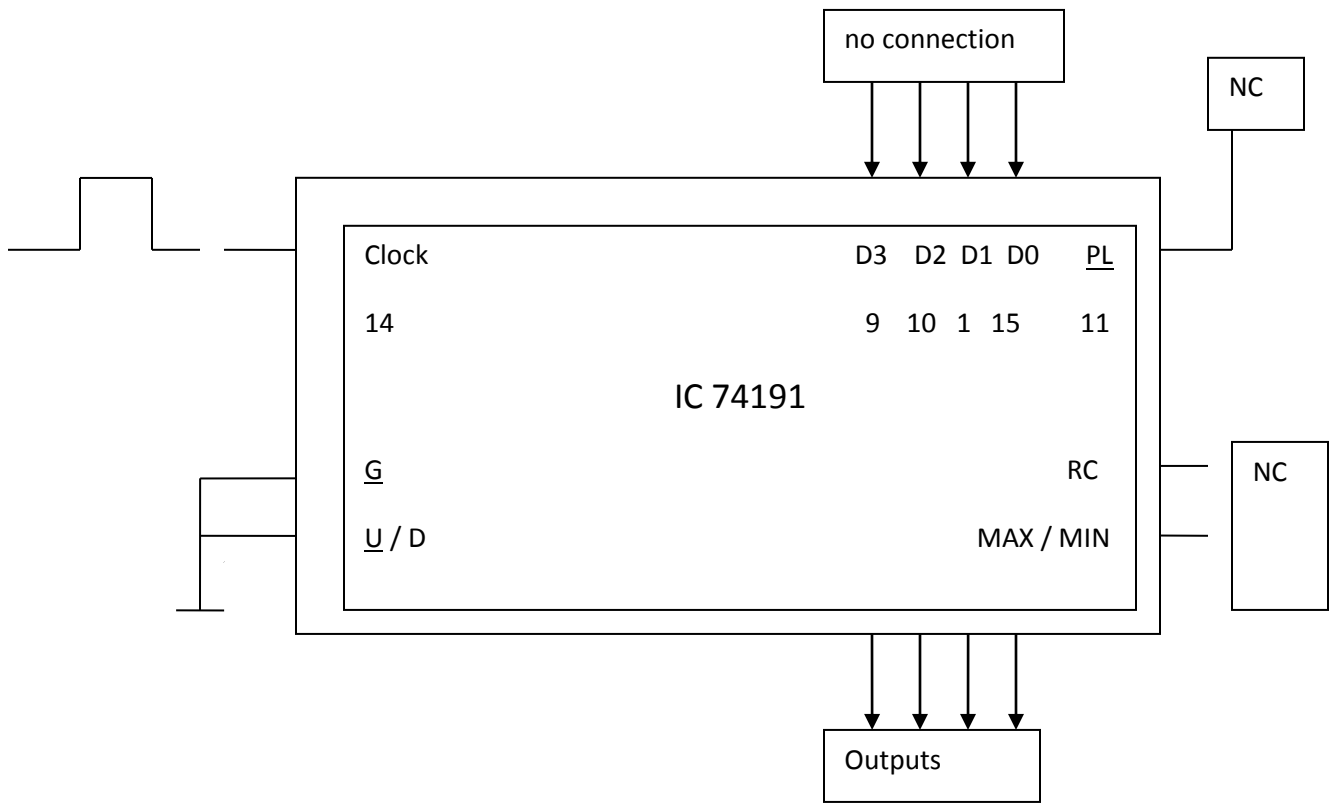


Steps-

- Connect the circuit as shown above.
- Apply clock i/p to pin no.14
- Connect U/D to GND.
- Verify the output according to truth table.

5. Modulus n Counter

Down counter- Truth Table

CLK Pulses	Q3	Q2	Q1	Q0
0	1	1	1	1
1	1	1	1	0
2	1	1	0	1
3	1	1	0	0
4	1	0	1	1
5	1	0	1	0
6	1	0	0	1
7	0	0	0	0
8	0	1	1	1
9	0	1	1	0
10	0	1	0	1
11	0	1	0	0
12	0	0	1	1
13	0	0	1	0
14	0	0	0	1
15	0	0	0	0

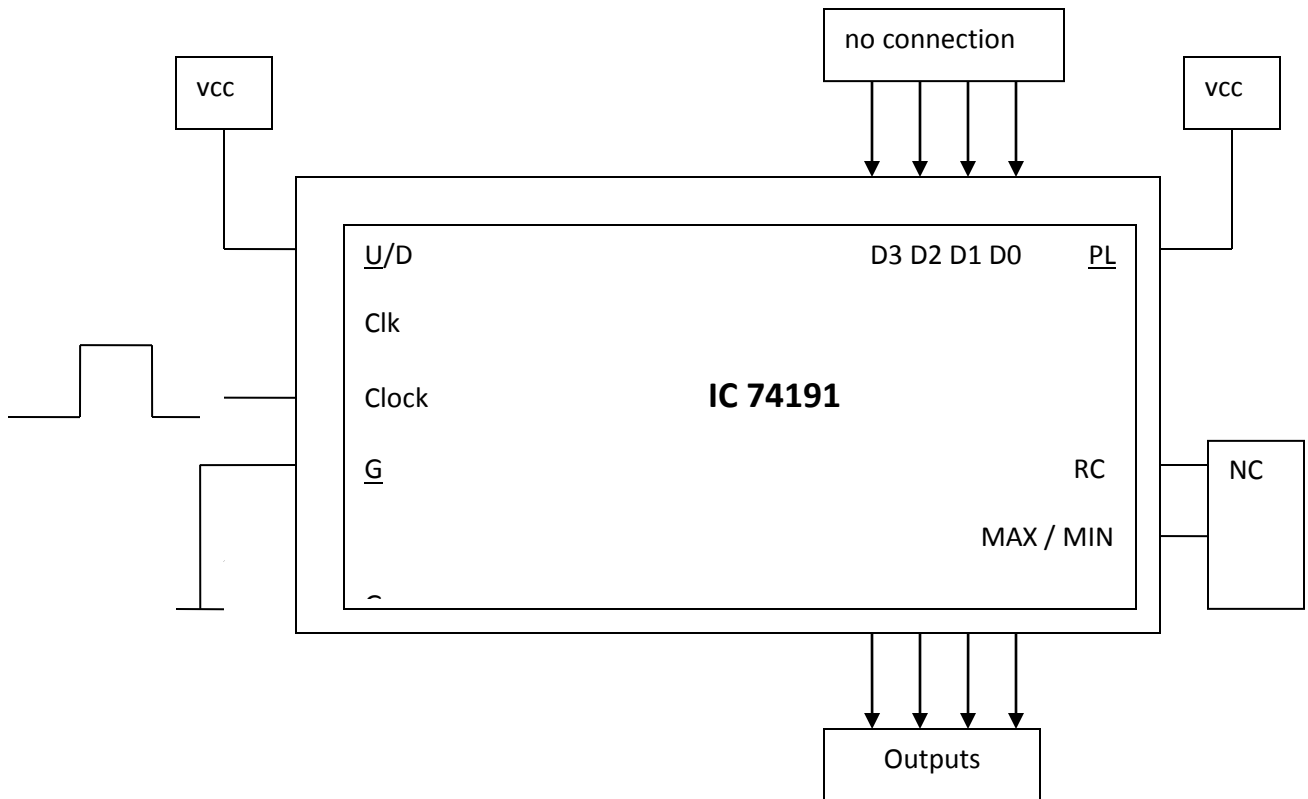

Logic diagram of down counter


Steps-

- Connect the circuit as shown above.
- Apply clock i/p to pin no.14
- Connect U/D to VCC.
- Verify the output according to truth table.

With the help of IC74191 we can implement **truncated up/down counter** by using following logic –

- Connect data input line to particular count you want to load
- According to requirement make Truth table
- Draw the K-map
- Find out Boolean expression
- Draw the logic diagram and that is the combinational logic for your count and apply the output of that circuit to PL
- According to requirement we get the UP and down counting

Presettable up/down counter

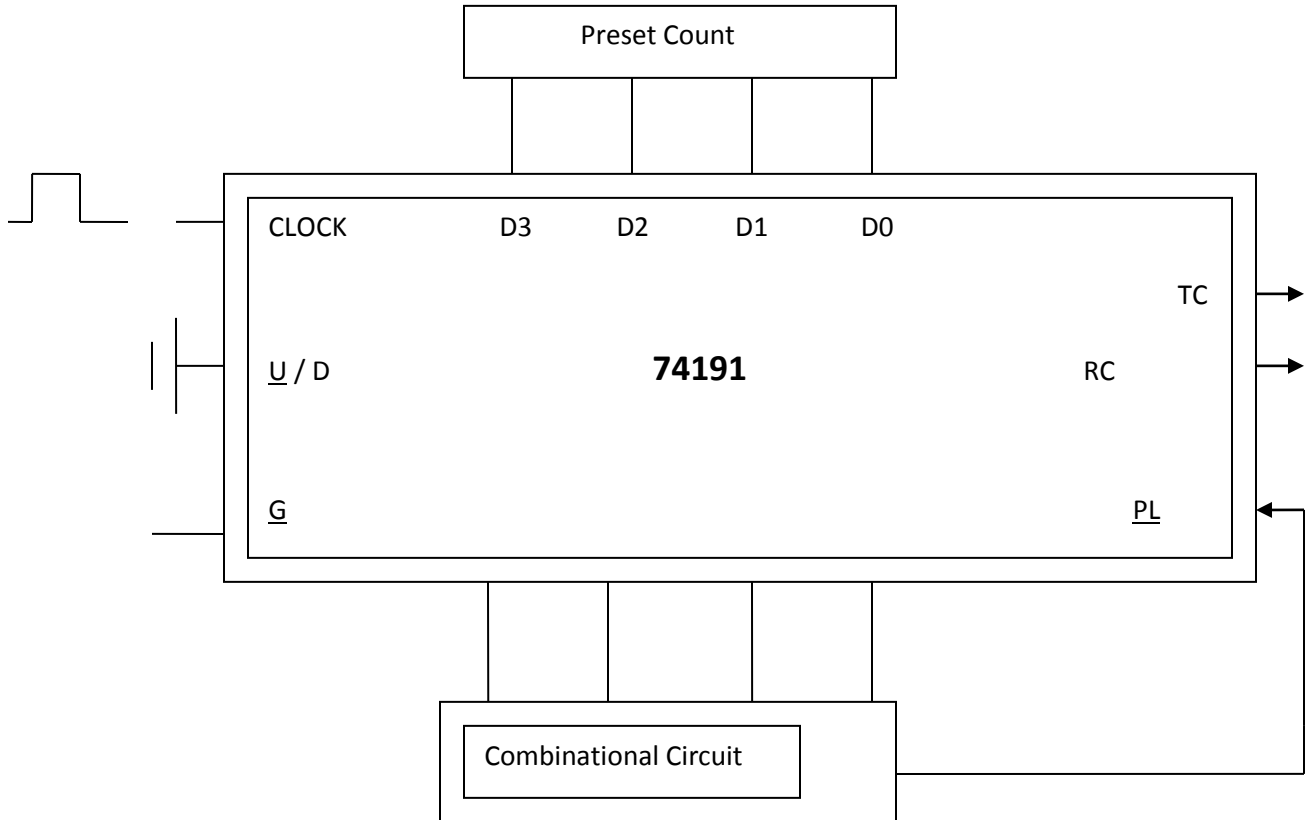

Mod 11 counter

Implementation of presettable mod up/down counter using IC- 74LS191

1. Load Data on data lines D0 to D3 (0101).
2. Counter will go through the states from 0101, 0110, ... 1111 in up counter and 0101 to 0000 in down counter.
3. The logic circuit should be designed in such a way that only when all the outputs are high, output of the reset circuit should be low and the counter should jump to state 5. It should again start counting from 0101 to 0000,


State Table**Down Counter**

Counter state / Clock pulse	F/F outputs			
	Q ₃	Q ₂	Q ₁	Q ₀
1	0	1	0	1
2	0	1	0	0
3	0	0	1	1
4	0	0	1	0
5	0	0	0	1
6	0	0	0	0
7	0	1	0	1

UP Counter

Counter state / Clock pulse	Q ₃	Q ₂	Q ₁	Q ₀
1	0	1	0	1
2	0	1	1	0
3	0	1	1	1
4	1	0	0	0
5	1	0	0	1
6	1	0	1	0
7	1	0	1	1
8	1	1	0	0
9	1	1	0	1
10	1	1	1	1
11	1	1	1	1

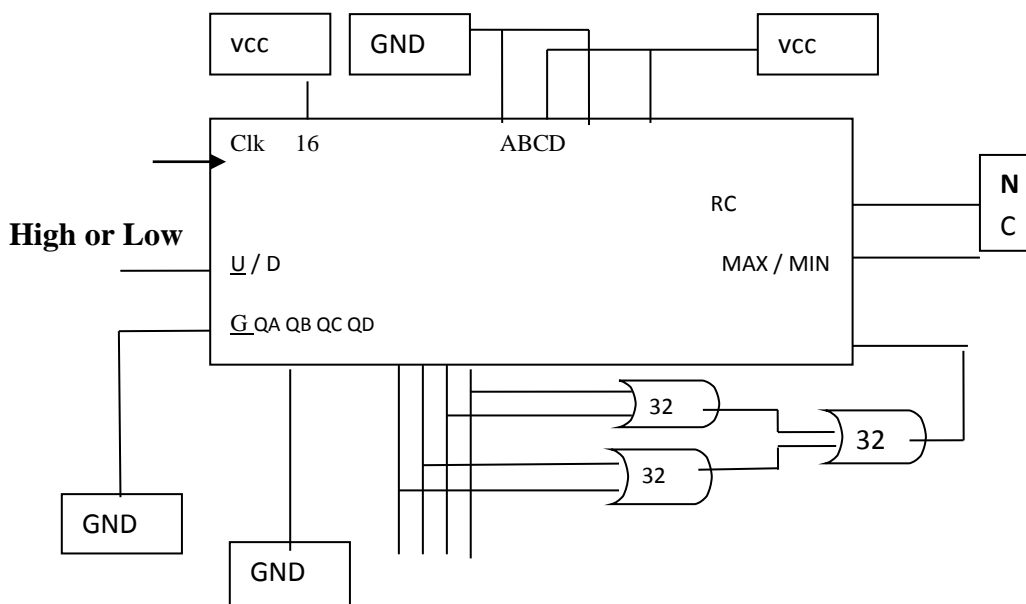IC 74191 is 4 bit counter. Thus it counts 0000 to 1111 different 16 states. For MOD11 counter we require different 11 states so 5 steps must be skipped from 16 states. We get MOD11 by presetting counter to value 5 .



FAQs:

- It represents the number of possible states of counter.

- The divide by 5 circuit followed by divide by 2 circuit will give symmetrical output.

- 1. Where counters are used? Give real life example of counter.**

5. Modulus n Counter

Binary counter – An N stage counter that recycles after 2^N count. The count proceeds in specified binary sequence.

5. Counter, Presetable- A counter which can be set to a desired value before the start of the counting/

6. UP/Down counter – A counter that can count in both up and down direction depending upon a control input.

6. Sequence Generator

AIM : To design and implement sequence generator with and without bushing using JK Flip flop IC 7476 & Shift Register IC 74194.

OBJECTIVE : To understand sequence generator, one of the sequential circuit.

IC's USED : IC 74194, 7408 (AND-gate), 7432 (OR-gate).

THEORY :

Part A. Sequence Generator with Flip flop

A sequential circuit which generates a prescribed sequence of bits in synchronism with a clock is referred to as a sequence generator. These pulse trains or sequence of bits can be used to open valves, close gates, turn on lights, and turn off machines and other variety of jobs.

For the design of sequence generator, we first determine the required no. of flip flops and the logic circuit for the next state decoder.

No. of flip flops required to generate particular sequence can be determined as follows.

- 1) Find the no. of 1's in the sequence.
- 2) Find the no. of 0's in the sequence.
- 3) Take the maximum out of two.
- 4) If N is the required no. of flip flops, choose minimum value of 'n' to satisfy equation given below.

$$\text{Max (0's , 1's)} \leq 2^{n-1}$$

The sequence generator can be classified as

- 1) sequence generator without bushing
- 2) sequence generator with bushing

The aim in this experiment is to design a sequence generator to generate a sequence of bit i.e. 10101.

Part B. Sequence Generator using Shift Register IC 74194

Theory : **IC 74194 : 4 bit bidirectional Shift Register:**

This bidirectional shift register is designed to incorporate virtually all the features a system designer may want in a shift register; they feature Parallel inputs, parallel outputs, right shift, left shift serial inputs, operating mode control inputs, and a direct overriding clear line. The register has four distinct modes of operations, namely:

Parallel load,

Shift right (in the direction QA towards QD)

Shift left (in the direction QD towards QA)

Inhibit clock (do nothing)

Synchronous parallel loading is accomplished by applying the four bits of data and taking both mode control inputs, S0 and S1, High. The data is loaded in to the associated flip-flops and appear at the outputs after positive transition of the clock input. During loading, serial data flow is inhibited.

Shift right is accomplished synchronously with the rising edge of the clock pulse when S0 is High and S1 is Low. Serial data for this mode is entered at the shift right data input. When S0 is Low and S1 is High, data shifts left synchronously and new data is entered at the shift left serial input.

Clocking of the flip flop is inhibited when both mode control inputs are LOW.

Mode Control Input		Operation
S1	S0	
0	0	Clock Inhibit
0	1	Shift right
1	0	Shift Left
1	1	Parallel loading

Function Table of IC 74194

Design:

The minimum number of flip-flops, N, required to generate a sequence of length S is given by $S \leq 2^N - 1$.

In this case S=7, therefore the minimum value of N, which may generate in this sequence is 3. However, it is not guaranteed to lead to a solution. If the given sequence leads to seven distinct

states, then only three flip flops are sufficient otherwise we have to increase the number of flip flops. We write the states of circuit as given in table 1. The prescribed sequence is listed under QA and the sequence listed under QB and QC are the same sequence delayed by one and two clock pulses respectively. From the table we observe that all the states are not distinct, which means $N=3$ is not sufficient. Next we assume that $N=4$ and prepare table 2. The last column gives the required serial input for getting the desired change of state when a clock pulse is applied. This is obtained by assuming D type flip flop and looking at the QA output. For example, at the falling edge of first clock pulse, QA=1. The second clock pulse must result in QA=1 which requires its D input to be 1. In the same manner, all the entries in column Y are determined.

Table 1. State Assignment Table of Sequence Generator ($N=3$)

Number of Clock Pulses	Flip Flop Inputs			States
	QA	QB	QC	
1	1	1	1	7 *
2	1	1	1	7 *
3	0	1	1	3
4	1	0	1	5 *
5	0	1	0	2
6	1	0	1	5 *
7	1	1	0	6

Excitation table of D Flip-Flop

Present State Q_n	Next State Q_{n+1}	Flip-Flop Input D
0	0	0
0	1	1
1	0	0
1	1	1

Table 2.State Assignment Table of Sequence Generator (N=4)


Number of Clock Pulses	Flip Flop Inputs				States	Y Serial i/p
	QA	QB	QC	QD		
1	1	1	1	0	14	1
2	1	1	1	1	15	0
3	0	1	1	1	7	1
4	1	0	1	1	11	0
5	0	1	0	1	5	1
6	1	0	1	0	10	1
7	1	1	0	1	13	1

K-Map Simplification:

	00	01	11	10
00	X	X	X	X
01	X	1	1	X
11	X	1	0	1
10	X	X	0	1

$$Y = QA' + QB' + QC' = \overline{QA.QB.QC}$$

LOGIC DIAGRAM:

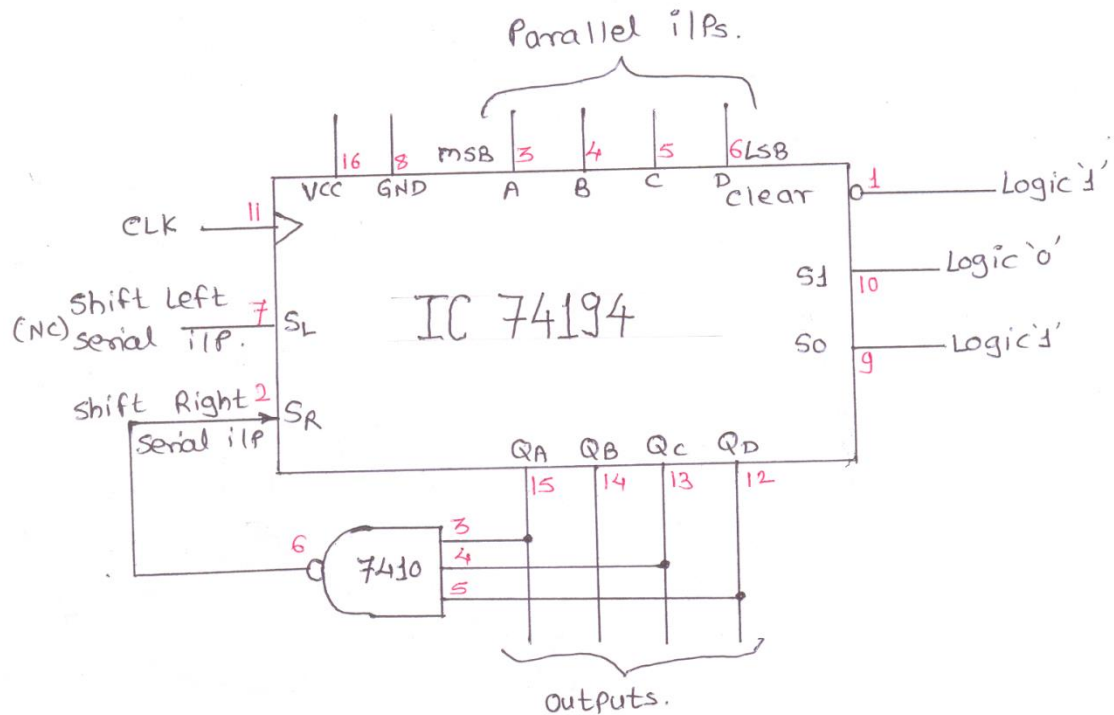

HARDWARE REQUIREMENTS:

Sl No.	ICs	Description	Quantity
1	74194	4 bit bidirectional universal shift register	1
2	7410	3 input NAND Gate	1

Conclusion: In this way sequence generator using JK flip flops & shift register is designed and implemented.

Enhancements / Modifications – Sequence generator can also be implemented with shift register instead of flip flops. Use IC 7495 universal shift register IC and try to implement sequence generator.

FAQs:

1. What is sequential logic circuit?

A sequential logic circuit consists of a memory elements in addition to combinational circuit. Its output at any instant of time depends upon the present input as well as present state of memory element.

2. What is meant by delay line?

It is used to introduce time delays in digital signals.

3. What is meant by following terms

- a) Synchronous preset b) Asynchronous preset
- c) Synchronous clear d) Asynchronous clear

- a)Preset operation is synchronised with the clock
- b)Preset operation is independent of the clock
- c) clear is performed in synchronous with clock
- d) clear is performed independent with clock

4. Is asynchronous counter faster than synchronous counter ?

In a synchronous counter the time required for change of any state is same and is equal to delay time of one flip flop where as in asynchronous counter all flip flops are not clocked simultaneously, hence time required is not same.

5. What is mean by lockout in counter?

In a counter design for a fewer state than the maximum possible state some time it may so happen that counter enters in unused state and goes from one unused state to another unused state and never comes to used state.

6. What is mean by state table?

It consists of complete information about present state and next state and outputs of a sequential system.

7. What is mean by state diagram?

The information available in a state table can be represented as graphically. the graphical representation is known as state diagram.

8. What is the advantage of state reduction in the design of sequential circuit?

It reduces the number of flip flops

9. What is meant by excitation table?

This gives information about what should be the flip flop inputs if outputs are specified before and after the clock pulse.

10. How many flip flops are required to design sequence generator using Counters:

$$\max(0^S, 1^S) \text{ in a given sequence } \leq 2^{(N-1)}$$

Where, N = Number of flip flops

11. How many flip flops are required to design sequence generator using shift registers:

$$S \leq 2^N - 1$$

Where, N=Number of flip flops

S= Length of sequence

12. What is Lock out condition? How it is avoided?

When counter enters into one of the invalid state and after application of pulses remains in invalid states only i. e. counter gets locked into invalid state & this is called as lock out. Lock out can be avoided by providing bushing to all the invalid states in such a way that after application of one or more clock pulses counter will fall into one of the valid state.

7. 4:1 Multiplexer using Data flow modeling.

AIM : -Simulation of 4:1 mux using data flow modeling.

OBJECTIVE: - To learn data flow modeling style. Its uses and different types of declarations with some different types of circuits. Structure of VHDL program is well discussed with this modeling style.

THEORY :-


Data flow style:-

In this type of design, the view of data as flowing from input to output through a design.

An operation is defined in terms of a collection of data transformation expressed as concurrent statement. Each of the statement can be activated when any of its input signal changes its value. While these statements describe the behavior of the circuit, a lot of information about its structure can be extracted from the description as well.

Data flow modeling has a set of concurrent assignment statements. In the data flow level of abstraction we describe how information is passed in the circuit. The built in operators in VHDL are used in expression such as AND, OR, XOR, NOT, etc.

Functional block diagram of 4:1 Mux:

 

7. 4:1 Multiplexer using Data flow modeling

Function table of 4:1 Mux:

$\overline{\text{Enable}}$	S1	S0	A	B	C	D	Y
1	X	X	X	X	X	X	0
0	0	0	A	X	X	X	A
0	0	1	X	B	X	X	B
0	1	0	X	X	C	X	C
0	1	1	X	X	X	D	D


Design steps:

- Click on Xilinx ISE 9.2i.
- Create New project from file menu. Ensure top level source is HDL.
- Select family of devices (usually spartan2E or 3)
- Ensure preferred language is VHDL.
- Click new source which shows you project details, device details and Synthesis and simulator tools.


- After finishing project create new source by right clicking in project name with VHDL module.
- Complete ports name, directions and bus. Ensure architecture name is behavioral.
- After that we will get design summary and detailed reports.
- Close design summary.
- Create your code with given modeling style.
- Go to process window and synthesis to check if any error is there in code. Check syntax and view RTL schematic.
- Create new source to simulate the code.
- Right click on source name and create test bench waveform with proper name. Ensure the project is same.
- Click on combinational circuit in initial timing wizard.
- Select test bench wave in source window. Apply inputs to wave diagram. Ensure you are in behavioral simulation.
- Go to process box. Click on Xilinx ISE simulator and simulate the model. See results.

7. 4:1 Multiplexer using Data flow modeling

RTL Schematic:

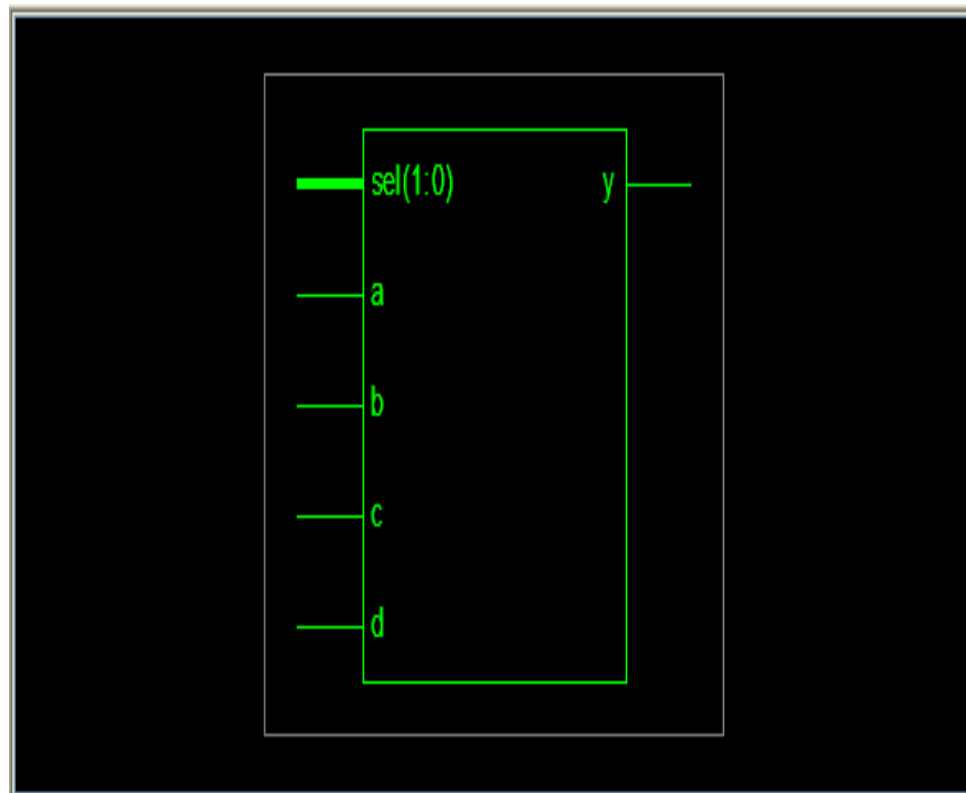

Timing Diagram:

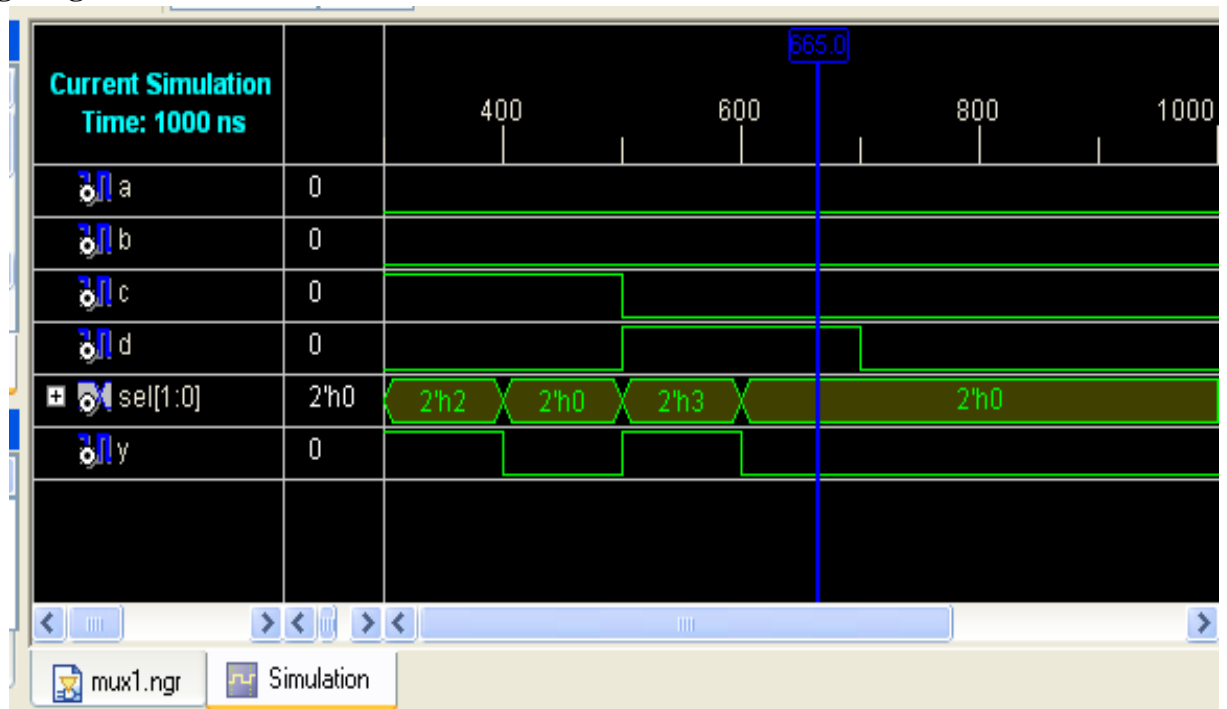

7. 4:1 Multiplexer using Data flow modeling

INPUT:

- Two select lines, S1,S0
- Four data lines, D0, D1, D2, D3

OUTPUT:

- One output line, Y

FAQ's:

1. What are the different kinds of data objects in VHDL code?

Ans: data object may be any value or number; still some signal data objects and bit and bit_vector types of these are available in VHDL. STD_LOGIC and STD_LOGIC_VECTOR types are used widely in programming.

2. What do you mean by signal?

Ans: signal is a data object represents logic signals or wires in a circuit. There are three places in which signals can be declared in VHDL code: in an entity declaration, in the declarative section of architecture, and in declarative section of package.

3. What are different signal types?


Ans: BIT, BIT_VECTOR, STD_LOGIC, STD_LOGIC_VECTOR, STD_ULOGIC, SIGNED, UNSIGNED, INTEGER, ENUMERATION, and BOOLEAN.

4. What is an *entity*?

Ans: a circuit or sub circuit described with VHDL code is called a design entity.

 5. Explain structure of an *entity*.

Ans: it has two main parts: the entity declaration, which specifies the input and output signals for entity, and the architecture, which gives circuit details.



6. How will you declare a package with component? Explain structure?

The general form of package declaration is as shown in diagram.

7. 4:1 Multiplexer using Data flow modeling

PACKAGE package_name IS

```
[TYPE declarations]

[SIGNAL declarations]

[COMPONENT declarations]

END package_name;
```

PRACTICE ASSIGNMENTS:

1. Implement 8:1 Mux using data flow modeling.
2. Implement 8:1 mux using 4:1 mux.
3. Implement 4:16 decoder using data flow style.
4. Implement active high 3:8 decoder.
5. Write VHDL code for decimal to BCD Encoder.

8. Full Adder using Structural modeling.

AIM : -Simulation of Full Adder using structural modeling.

OBJECTIVE: To learn structural modeling style. Its uses and different types of declarations with some different types of circuits. Structure of VHDL program is well discussed with this modeling style

THEORY :- Structural style:-

A digital electronic system can be described as a module with inputs and/or outputs. The electrical values on the outputs are same functions of the values of inputs. The example of it is as shown. The NAND gate has 2i/ps, A&B, & an output y. Using VHDL terminology, we call the NAND2 design entity & the inputs & outputs are called ports. 1 way of describing the function of NAND2 is to describe how it is composed of sub modules AND & INVERTER Each of the Sub modules is an instance of some entity & ports of the instances are connected using signals. Structural modeling has a set of interconnected component. Structure can be used to create a very low level description of a circuit or a very high level description.


In a gate level description of a circuit, for example components such as basic logic gates & F/Fs might be connected in some logical structure to create the circuit. This is what is often called a net list.

8. Full Adder using Structural modeling.

Structure of structural modeling:


```
architecture NetlistofHalf_Adder is
-- component with locals
component MyXorport (A_Xor,B_Xor : in BIT;
    Z_Xor : out BIT);
end component;
-- component with locals
component MyAndport (A_And,B_And : in BIT;
    Z_And : out BIT);
end component;
begin
    Xor1: MyXorport map (X, Y, Sum);
-- instance with actuals
```

Functional block diagram of Full Adder:

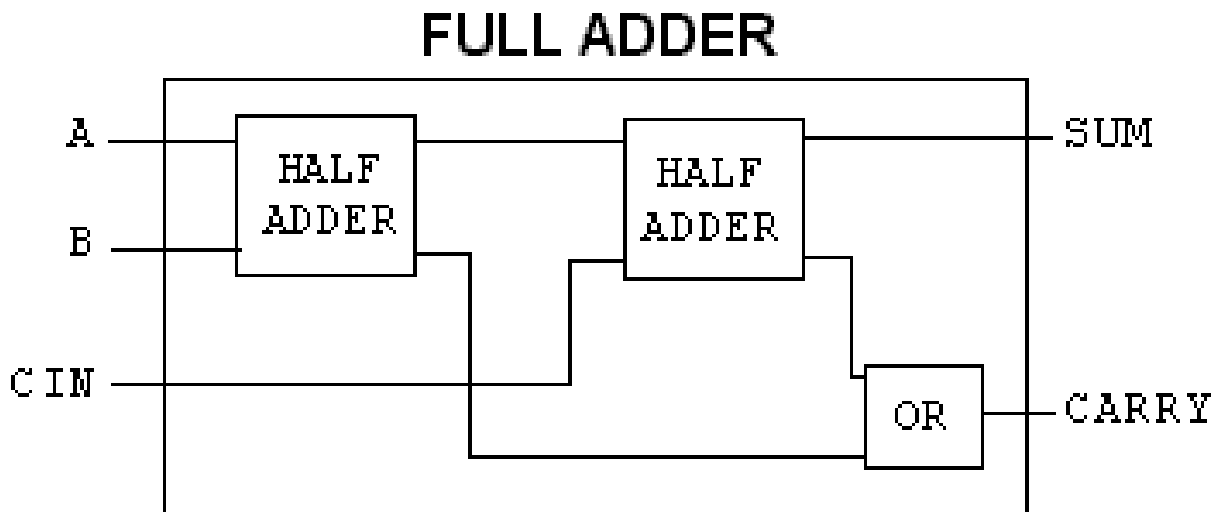

8. Full Adder using Structural modeling.

Function table of Full Adder:

A	B	Cin	SUM	CARRY
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$\text{Sum} = \Sigma m(1, 2, 4, 7)$$

$$\text{Carry} = \Sigma m(3, 5, 6, 7)$$

Design steps:


- Click on Xilinx ISE 9.2i.
- Create New project from file menu. Ensure top level source is HDL.
- Select family of devices (usually spartan2E or 3)
- Ensure preferred language is VHDL.
- Click new source which shows you project details, device details and Synthesis and simulator tools.
- After finishing project create new source(full adder) by right clicking in project name with VHDL module.
- Complete ports name, directions and bus. Ensure architecture name is behavioral.
- After that we will get design summary and detailed reports.
- Close design summary.
- Click new source which shows you project details, device details and Synthesis and simulator tools.
- After finishing project create new source(half adder) by right clicking in project name with VHDL module.
-

8. Full Adder using Structural modeling.


- Complete ports name, directions and bus. Ensure architecture name is behavioral. Names should be same as previous inputs.
- After that we will get design summary and detailed reports.
- Close design summary
- Create your code for half adder with given modeling style.
- After that go to process window. Click on design utilities.
- View HDL instantiation code of half adder.
- Copy component part of half adder in architecture block of full adder. Copy instantiation template twice after begin as we require two half adders to construct full adder (structural modeling). Name them differently (e.g. ha1 or ha2).
- Create signals as per the logic. Complete code of full adder.
- Go to process window and synthesis to check if any error is there in code. Check syntax and view RTL schematic.
- Create new source to simulate the code.
- Right click on source name and create test bench waveform with proper name. Ensure the project is same.
- Click on combinational circuit in initial timing wizard.
- Select test bench wave in source window. Apply inputs to wave diagram. Ensure you are in behavioral simulation.
- Go to process box. Click on Xilinx ISE simulator and simulate the model. See results.

8. Full Adder using Structural modeling.

RTL Schematic:

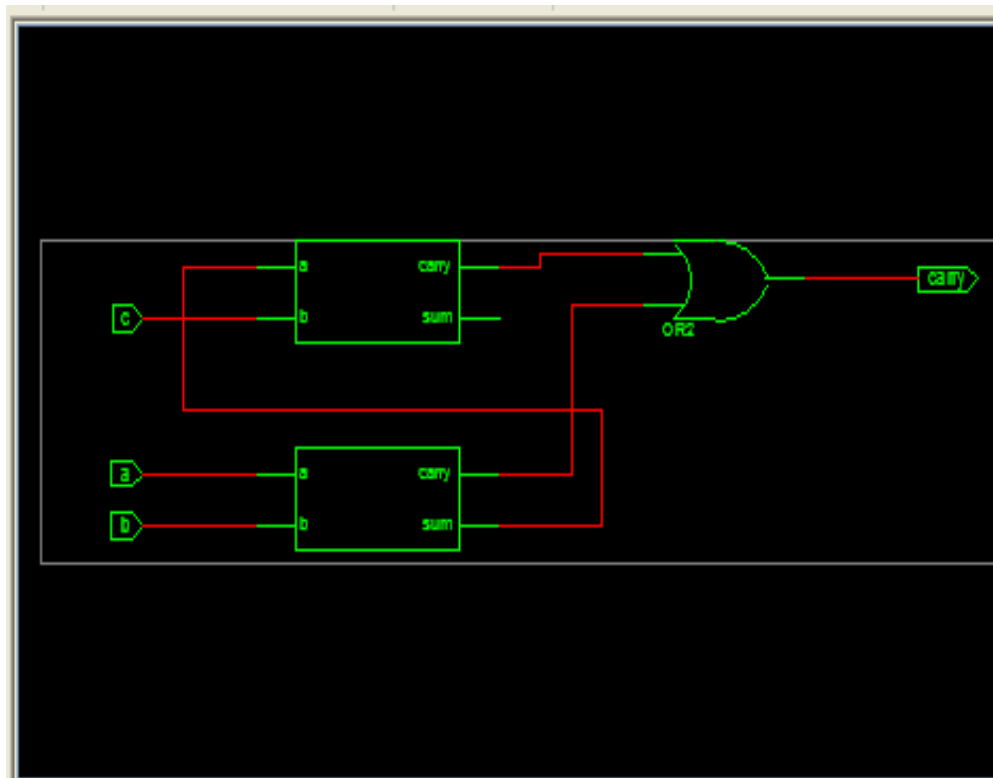

Timing Diagram:

 

8. Full Adder using Structural modeling.

INPUT:

- Three inputs A, B, Carry (previous)

OUTPUT:

- Two outputs Sum, Carry

FAQ's:

1. What do you mean by structural style?

Ans : in this type of code a circuit is described in hierarchical fashion, by connecting together sub circuits.

2. Explain IF statement with example.

Ans: The general form of an IF statement is as follows:

IF Sel='0' THEN

F<=x1;

ELSE

F<=x2;

END IF;

3. Explain declaration and instantiation process in VHDL.

Ans: first declare a small vhd code in formal way. E.g. half adder. Define project name is full adder. And simply copy instantiation template in main source code. Define how many times you want to declare this template. Give separate names for those.

4. What is STD_LOGIC_VECTOR?

Ans: It is standard data object added to VHDL standard in IEEE 1164. It provides more flexibility than the Bit type.

5. Explain difference between concurrent and sequential statements?

Ans: Concurrent statements define interconnected processes and blocks that together describe a design's overall behavior or structure. They can be grouped using block s13.

8.Full Adder using Structural modeling.

tatement. Groups of blocks can also be partitioned into other blocks. At this same level, a VHDL component can be connected to define signals within the blocks.

It is a reference to an entity. A process can be a single signal assignment statement or a series of sequential statements (SS). Within a process, procedures and functions can partition the sequential statements

PRACTICE ASSIGNMENTS:

1. Implement half adder using data flow modeling.
2. Implement Full Adder using behavioral modeling.
3. Implement 3 bit magnitude comparator using a 3 bit adder.
4. Implement half sub tractor using data flow modeling.
5. Write VHDL code for Full Subtractor.

9. 3bit Controlled up / down synchronous counter with preset & clear.

AIM : -Simulation of 3 bit Counter using Behavioral modeling.

OBJECTIVE: To learn behavioral modeling style. Its uses and different types of declarations with some different types of circuits. Structure of VHDL program is well discussed with this modeling style

THEORY :-

Behavioral style:-

Highest level of abstraction supported in VHDL is called the behavior level of abstraction. In it we have for loop, while loop, If then else, case & variable assignment. The statements are enclosed in a PROCESS block, & are executed sequentially.

In it circuit is described in terms of its operation overtime.

In behavioral description, the concept of time may be expressed precisely, with actual delays between related events (such as the propagation delays within gates & on wires.) or it may be simply an ordering of operation that are expressed sequentially (such as in a functional description of a F/F).

A behavioral design method defines a circuit in terms of text language rather than a schematic of interconnected symbols.

Behavioral design is a technology independent, text based design that incorporates high level functionality & high level information flow.

Structure of Behavioral modeling:

```
architecture behave of and_gate is
begin
process (a, b)
begin
    if a = '1' and b = '1' then
        c <= '1';
    else
        c <= '0';
    end if;
end process;
end behave;
```

9. 3bit Controlled up / down synchronous counter with preset & clear.

Functional block diagram of 3 bit controlled up / down synchronous counter with preset & clear:

Function table of 3 bit controlled up / down synchronous counter with preset & clear:

Design steps:

- Click on Xilinx ISE 9.2i.
 - Create New project from file menu. Ensure top level source is HDL.
 - Select family of devices (usually spartan2E or 3)
 - Ensure preferred language is VHDL.
 - Click new source which shows you project details, device details
 - and Synthesis and simulator tools.
 - After finishing project create new source by right clicking in project name with VHDL module.
 - Complete ports name, directions and bus. Ensure architecture name is behavioral.
 - After that we will get design summary and detailed reports.
 - Close design summary.
 - Create your code with given modeling style.
 - Go to process window and synthesis to check if any error is there in code. Check syntax and view RTL schematic. Create new source to simulate the code
 - Right click on source name and create test bench waveform with proper name. Ensure the project is same.
 - Click on combinational circuit in initial timing wizard.
 - Select test bench wave in source window. Apply inputs to wave diagram. Ensure you are in behavioral simulation.
- Go to process box. Click on Xilinx ISE simulator and simulate the model.

RTL Schematic:

Timing Diagram

9. 3bit Controlled up / down synchronous counter with preset & clear.

INPUT:

- Clock, Preset, Clear

OUTPUT:

- Three output lines,

FAQ's:

1. Explain the structure of behavioral modeling?

```

architecture behave of and_gate is
begin
  process (a, b)
  begin
    if a = '1' and b = '1' then
      c <= '1';
    else
      c <= '0';
    end if;
  end process;
end behave;

```

2. What are the differences between behavioral and structural modeling?

Ans: Behavioral description of a circuit is the highest level of abstraction in VHDL. Here, the circuit is described in terms of its operation with respect to time. All operations are in one level of code. The operations are described in a way that the designer of a sequential circuit infers a register

Structural description, on the other hand, is a circuit description in terms of its components. It can either create a low level description, much like a hierarchy in a block diagram. Whenever you see a *component* instantiated in a code, that code employs structural description of the circuit. The components are connected in the form of a *netlist*. This is for better manageability and reusability

3. What are the differences between behavioral and data flow modeling?

Ans: Behavioral – describes how the output is derived from the inputs using structured statements.

Dataflow – describes how the data flows from the inputs to the output most often using NOT, AND and OR operations

4. What do you mean by *process* statement?

Ans: The process statement begins with the PROCESS keyword, followed by a parenthesized list of signals, called the sensitivity list. It operates on selected and conditional statements.

9. 3bit Controlled up / down synchronous counter with preset & clear.

5. Explain syntax of *process* statement?

Ans: BEGIN

Process(sensitivity list)

;

;

END process;

PRACTICE ASSIGNMENTS:

1. Implement 3 bit asynchronous up counter using behavioral modeling.
2. Implement 3 bit asynchronous down counter using behavioral modeling.
3. Implement 3 bit synchronous down counter using behavioral modeling.

APPENDIX

A. University Syllabus

214446: DIGITAL LABORATORY

Teaching Scheme
Practical: 2hrs / week

Credits : 01

Examination scheme
Practical: 50 Marks
TW : 25 Marks

Group A

Combinational Logic Design

1. Design (truth table, K-map) and implementation of 4-bit BCD to Excess-3 and Excess-3 to BCD Code converters.
2. Design (truth table, K-map) and implementation of 4 bit BCD & Excess 3 Adder using IC7483.
3. Implementation of logic functions using multiplexer IC 74153 & decoder IC 74138.
(Verification, cascading & logic function implementation)

Group B

Sequential Logic Design

1. Design (State diagram, state table & K map) and implementation of 3 bit Up and Down Asynchronous and Synchronous Counter using master slave JK flip-flop IC 7476
2. Design and implementation of Module 'n' counter with IC7490 and IC 74191.
3. Design (State Diagram, State Table, K Map) and implementation of Sequence Generator using Shift Register IC 74194.

Group C

VHDL Programming

Simulation of

1. 4:1 multiplexer using data flow & structural modeling.
2. Full adder using behavioral & structural modeling.
3. 3 bit controlled up / down synchronous counter with preset & clear

Group D

Design, construct digital logic circuits & analyze their behavior through simulation of any one assignment from either group A or Group B with simulation software like Digital works 3.0

Reference Books

1. "Modern Digital Electronics", R.P. Jain, 3rd Edition, Tata McGraw-Hill, ISBN: 0-07-049492-4
2. "Fundamentals of Digital Logic with VHDL Design", Stephen Brown, Zvonko Vranesic McGraw-Hill, ISBN: 978-0-07-352953-0
3. "Digital Logic applications and Design", John Yarbrough, Thomson Publication ISBN: 978-0314066756

Instructor will frame assignments based on the suggested assignments as given above. Students will submit the term work in the form of journal consisting of 9 assignments listed above. Practical examination will be based on practical assignments and questions will be asked to judge the understanding of assignments performed at the time of examination.

Note - Instructor should take care that datasheets of all the required ICs are available in the laboratory & students are verifying the functionality of ICs being used.


B. Assignment separator for the student's Journal.

Assignment No.:


Title :

C. Pin Diagrams


7400: Quad 2-Input NAND Gate

 


7402: Quad 2-Input NOR Gate

 


7404: Hex Inverting Gates

 


7408: Quad 2-Input AND Gates

 

7410: Triple 3-Input NAND Gate

 


7432: Quad 2-Input OR Gate

 


7474: Dual Positive Edge Triggered D Flip-Flop


Dual-In-Line Package

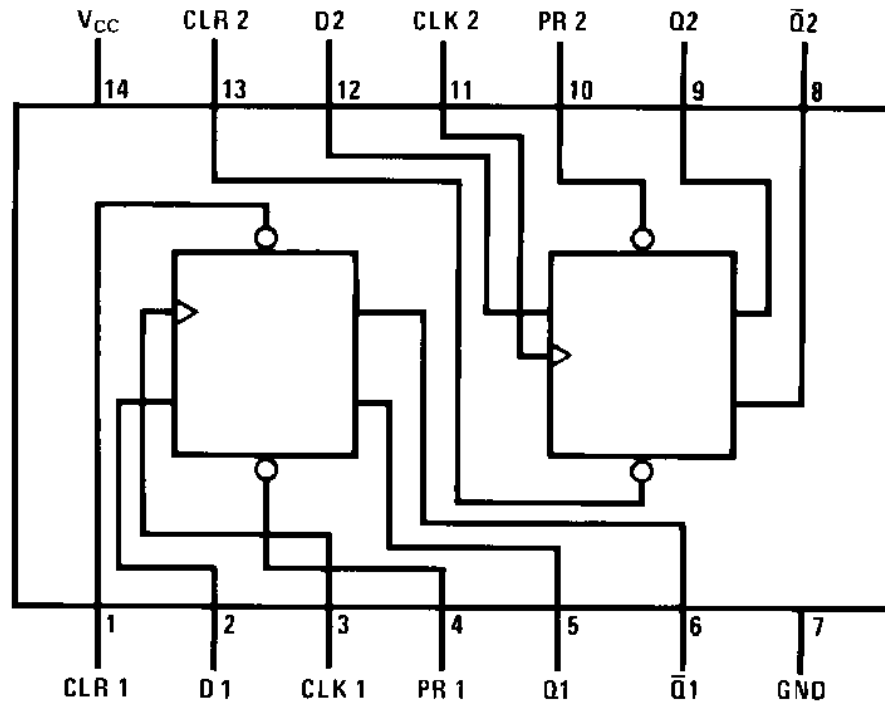


7476: Dual Master-Slave J-K Flip-Flops

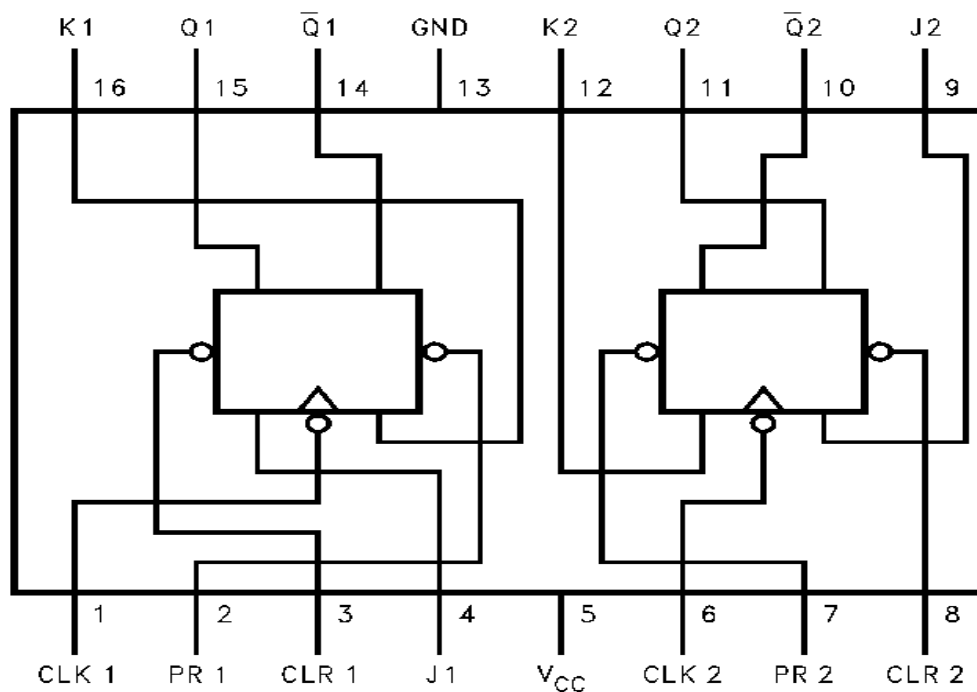


7483: 4 bit Binary Adder

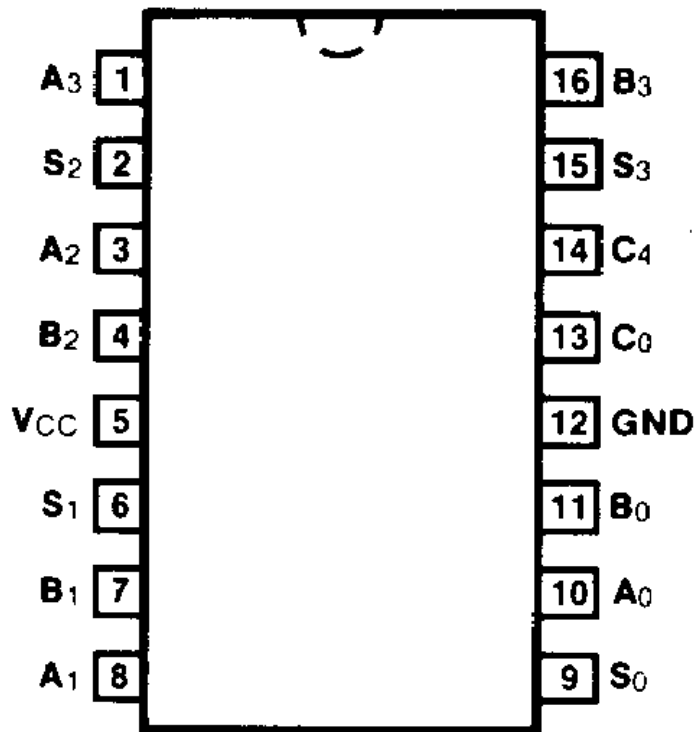


7486: Quad 2-Input Exclusive-OR Gate

 


7490: Decade and Binary Counters

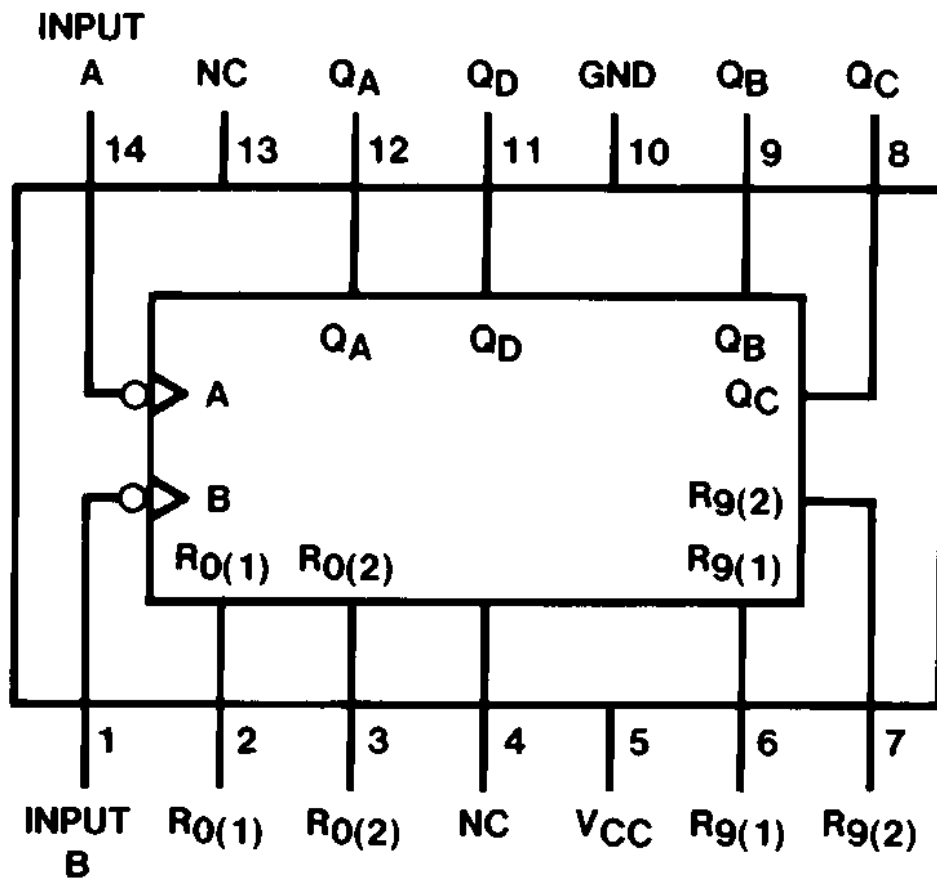


74138: 3:8 Decoder

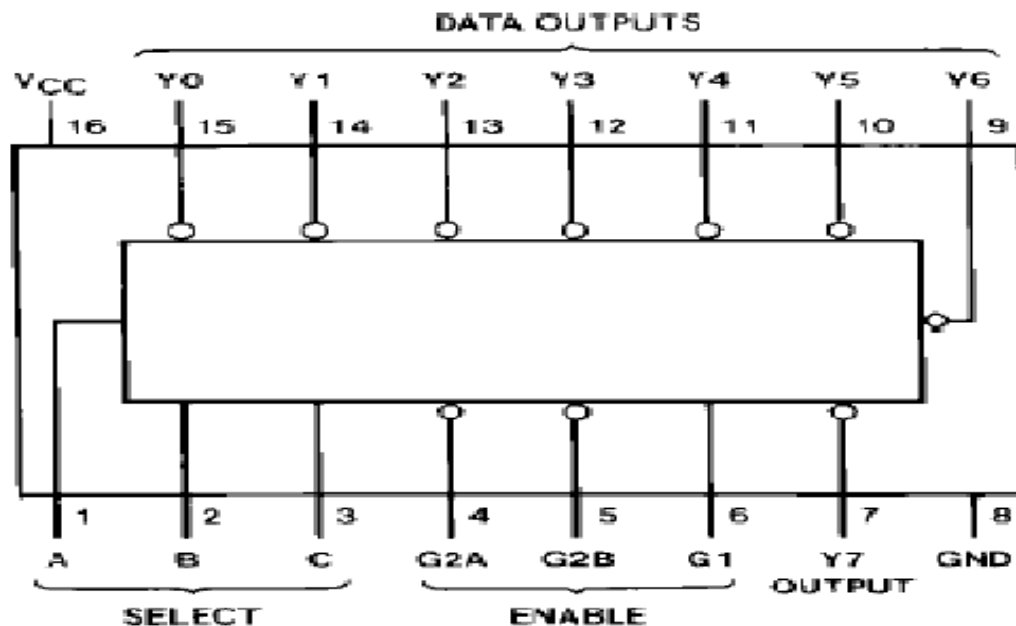


74151: 8:1 Multiplexer

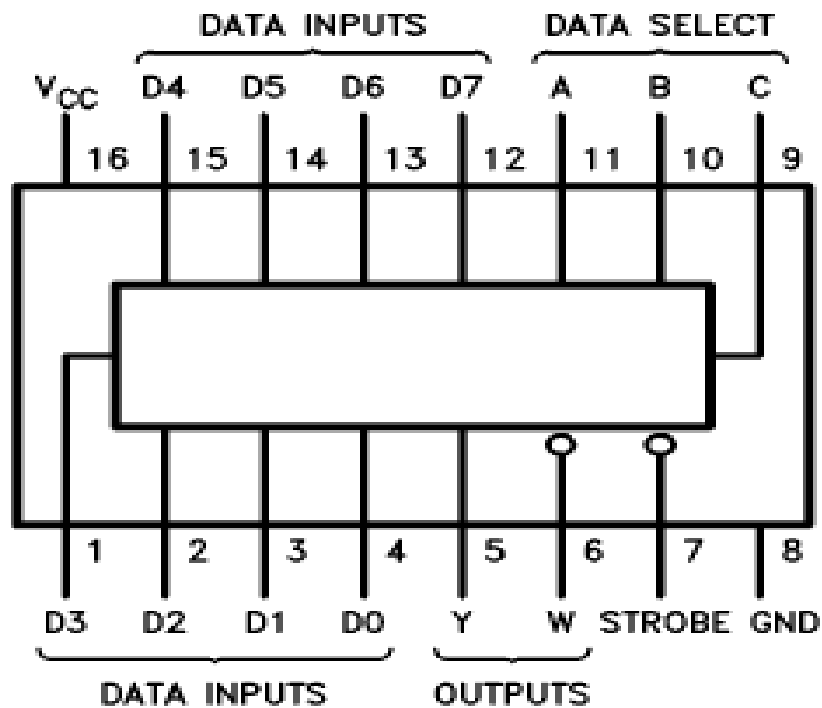


74153: Dual 4:1 Multiplexer

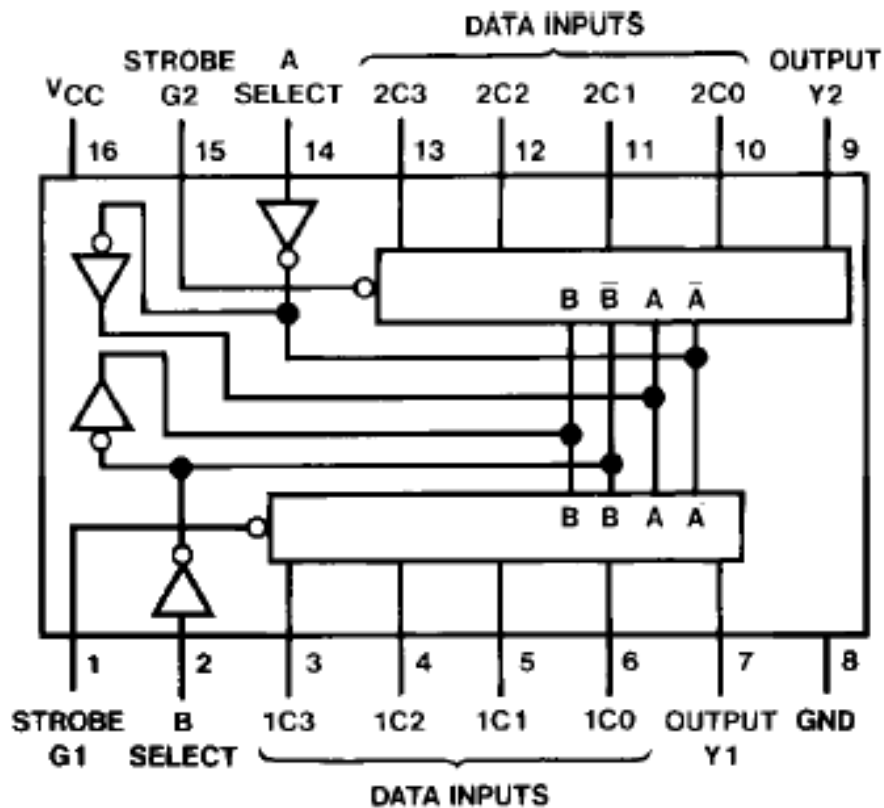

74180: 8 bit Parity Generator/Checker

 

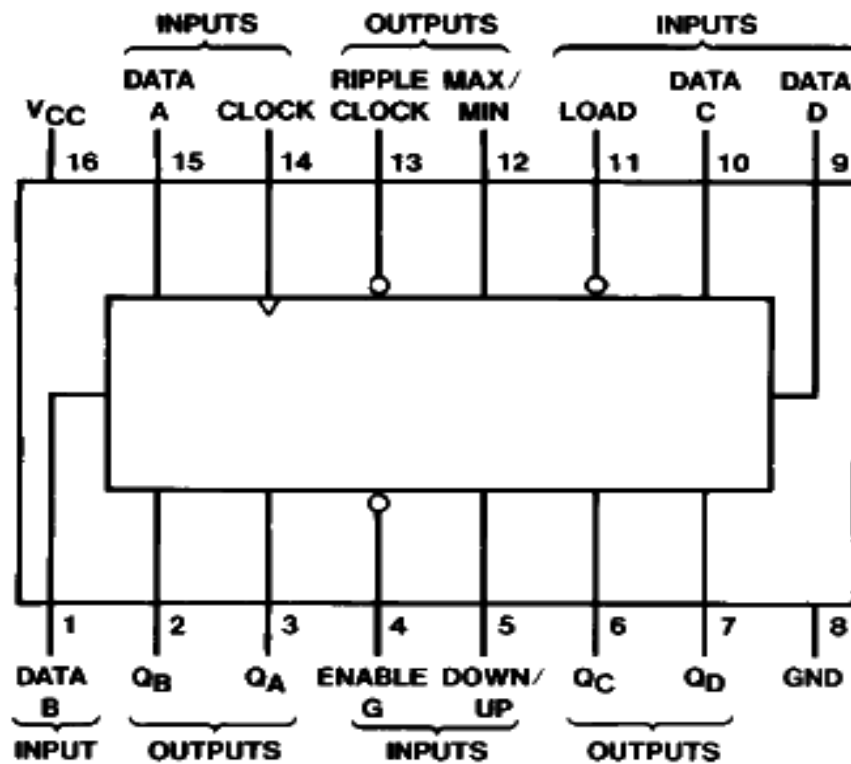74191: Synchronous Up/Down 4 bit Binary counter with Mode Control



74194: Universal Shift Register

